

# Circuit Wizardry Workshop #1

Presented by:  
Optics Society at the University of Michigan

# Safety

Electricity is really cool but can be dangerous. We are going to be working with small amounts of electricity. At home, your electronic devices and the wall use MUCH bigger amounts of electricity.

Number 1 Rule: *At home, experiment with your parent's supervision.*

# Where do we start?

What is electricity?

Is electricity manmade? In nature? Or both?  
(is lightning a form of electricity? How about static shock?)

Where does power come from?

Can a circuit be made from any material?

What do you know about electrons?



# Would This Work?



# Would This Work?



# Would this Work?





Watch:

<https://www.youtube.com/watch?v=Ww6xYGu3O10>


Discuss!

# The Central Concept: Closed Circuit





# Current

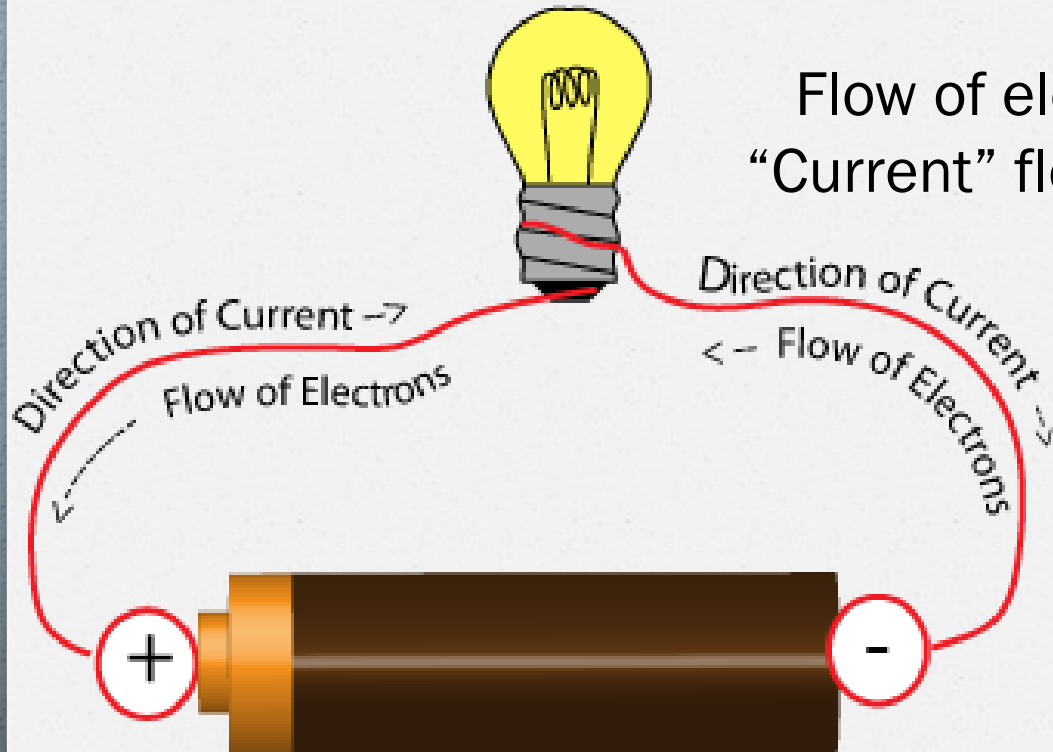

Flow of electrons (like a river)  
“Current” flows from (+) side of  
battery to (-) side

Electrons go the  
other way

# Conductor


Allows easy flow of electrons



Examples: Copper wire(shown in picture), paper clip, any metal  
Skin is a “weak” conductor
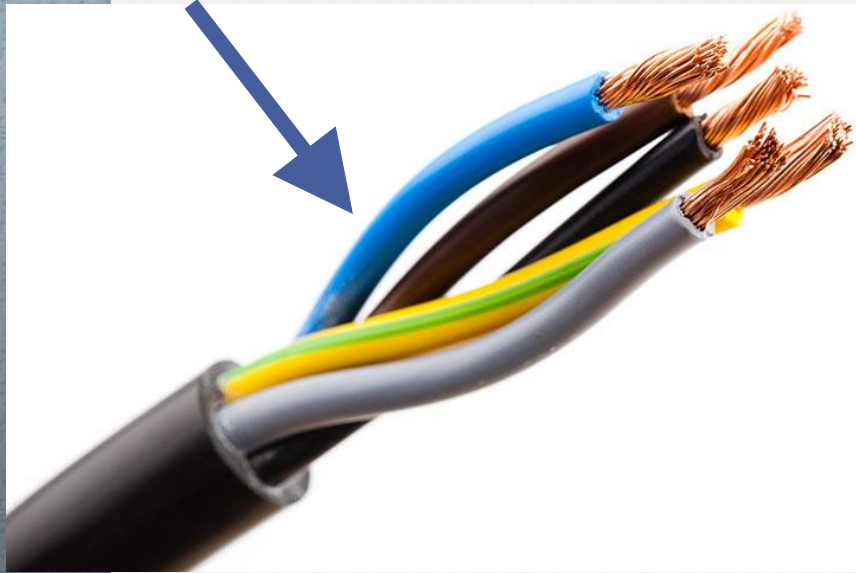
# Insulator

Does NOT allow electrons to flow at all. (No conduction)





Examples: Rubber (shown in picture), wood, cloth, plastic, cardboard



# Voltage

Voltage is like pressure (sort of)

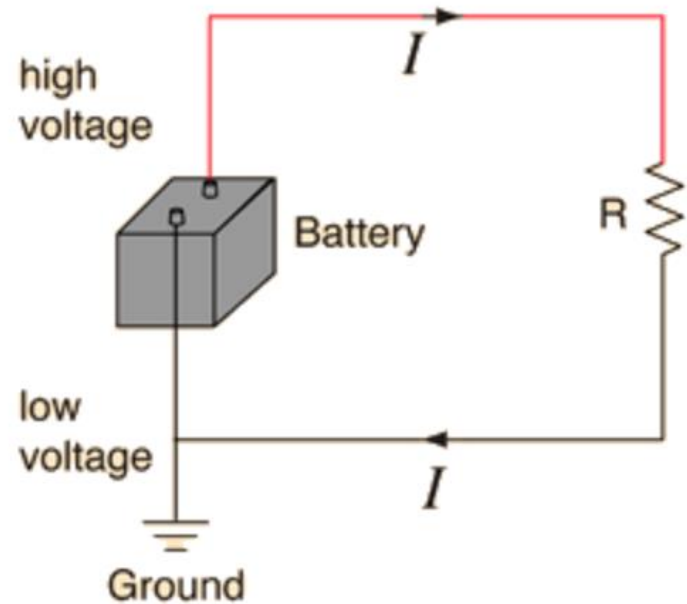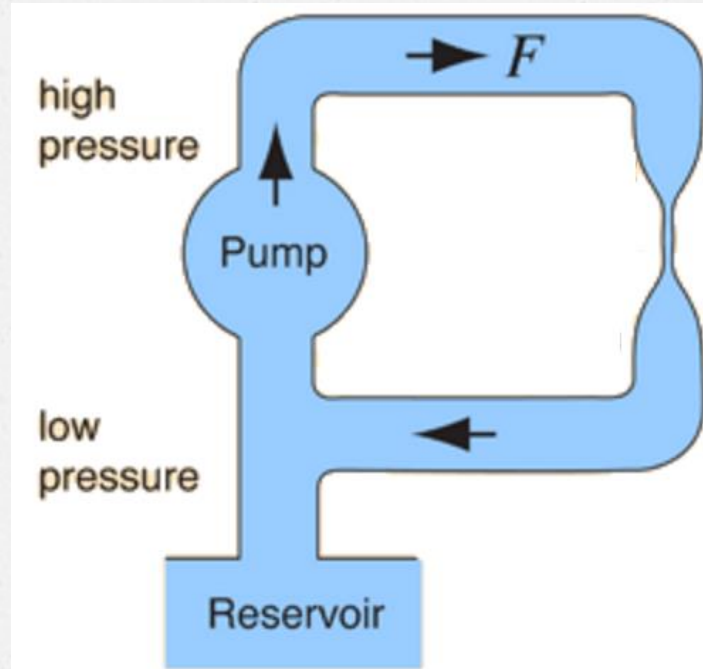





You Be the Electron!




Practice Practice Practice...



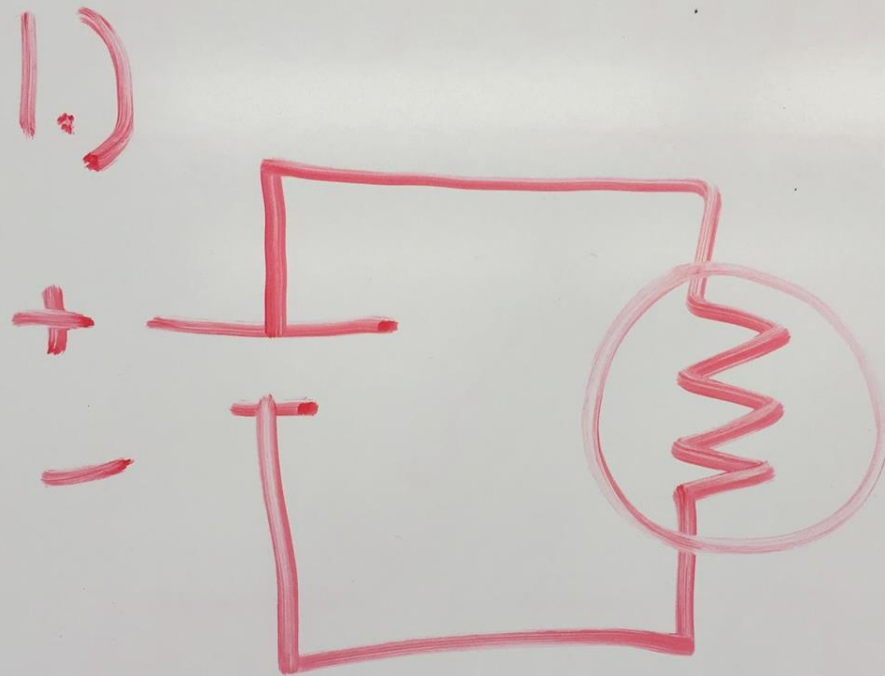

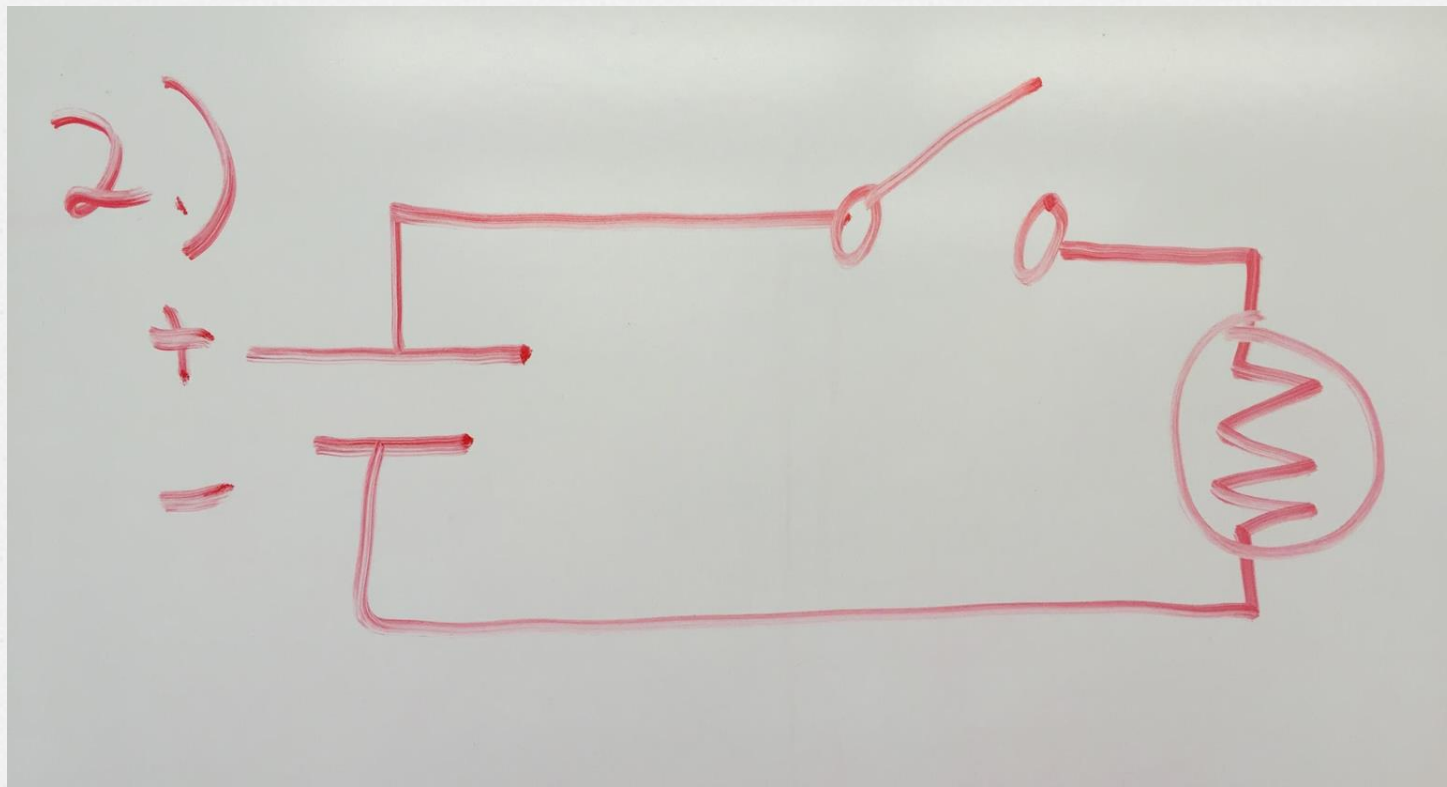



3.)

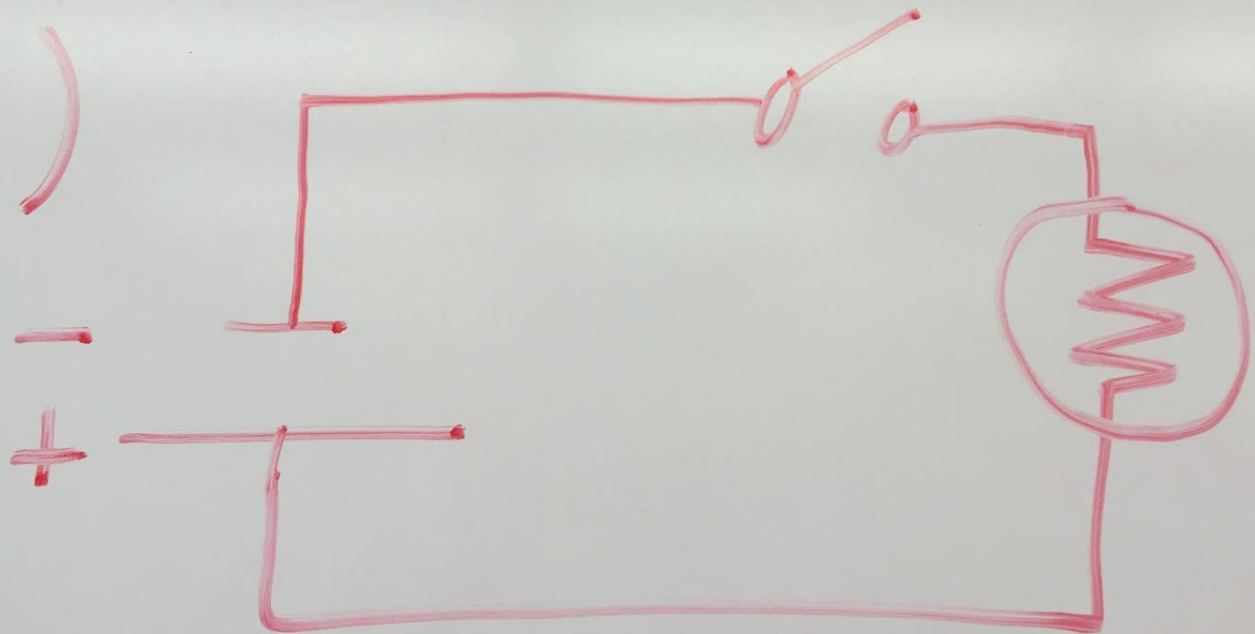



4.)

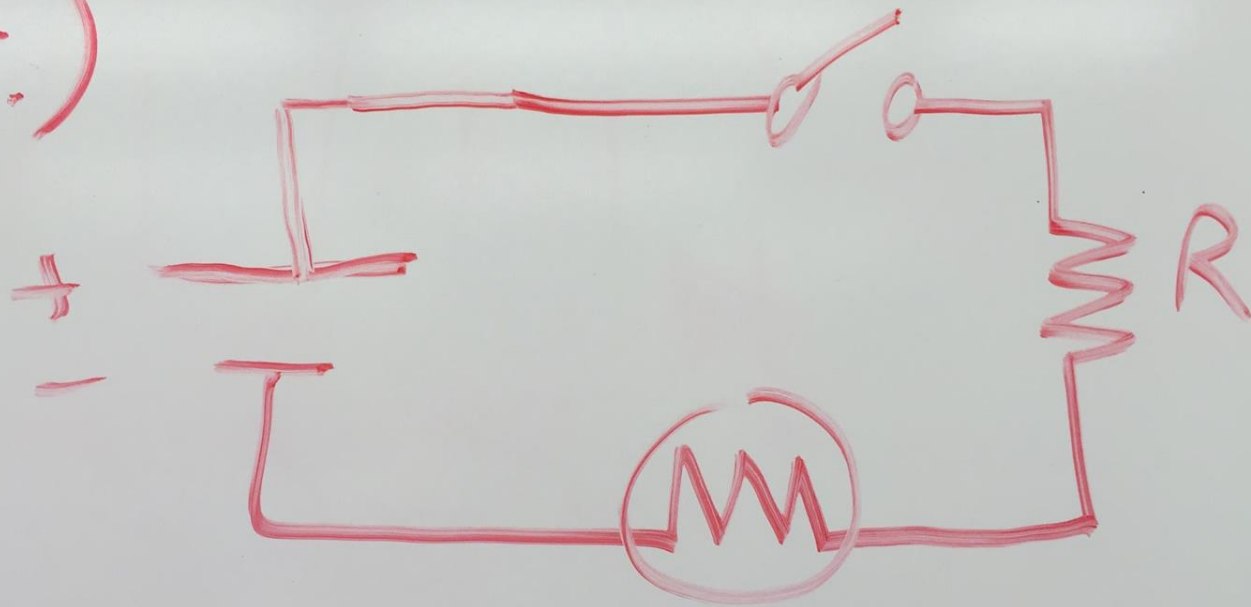

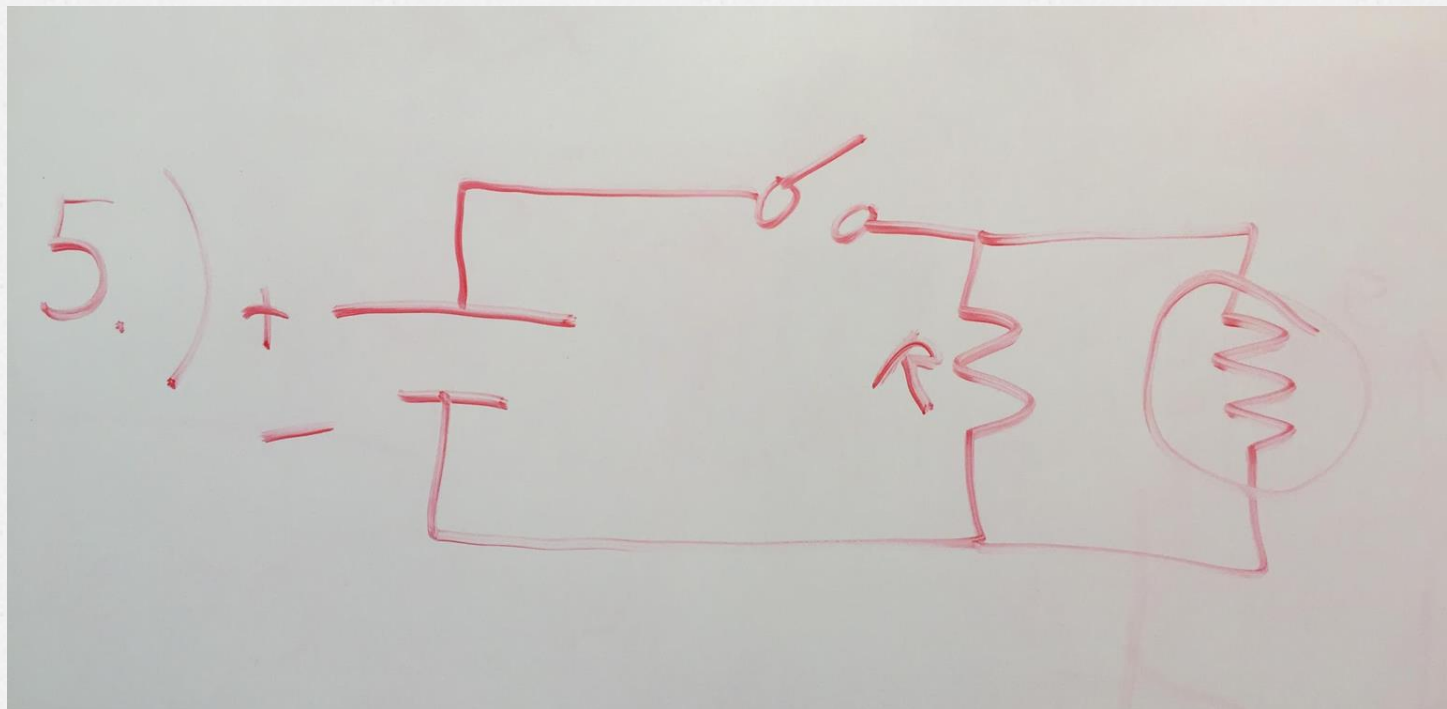



# Flashcards




# Wire with terminals



A wire must be a *conductor*  
It may or may not connect to  
anything.


# Junction

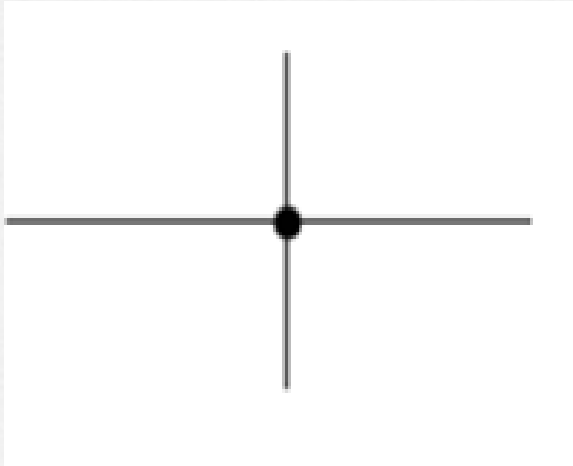

These two wires are connected.  
They act as one single wire
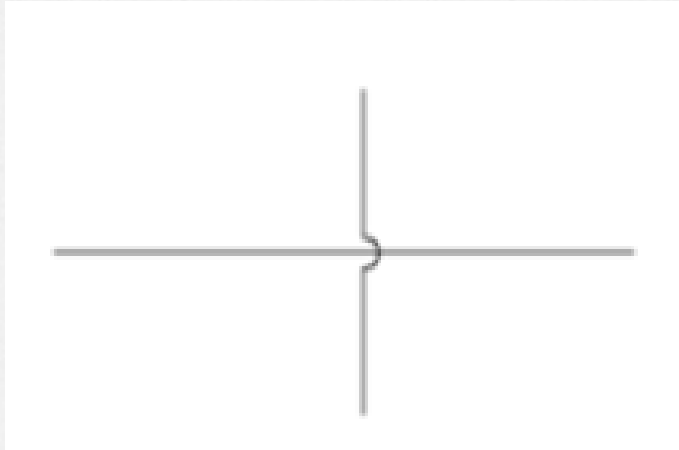
# Wire crossing (no connection)

Two completely separate wires -  
not touching.





# Battery

Provides energy to circuit.

It's the "starting line" and "finish line" for electrons.

The longer line is positive (+) side

The shorter line is negative (-) side




# Resistor

Slows down current  
Releases energy



# Lamp

Releases energy (as light and heat)

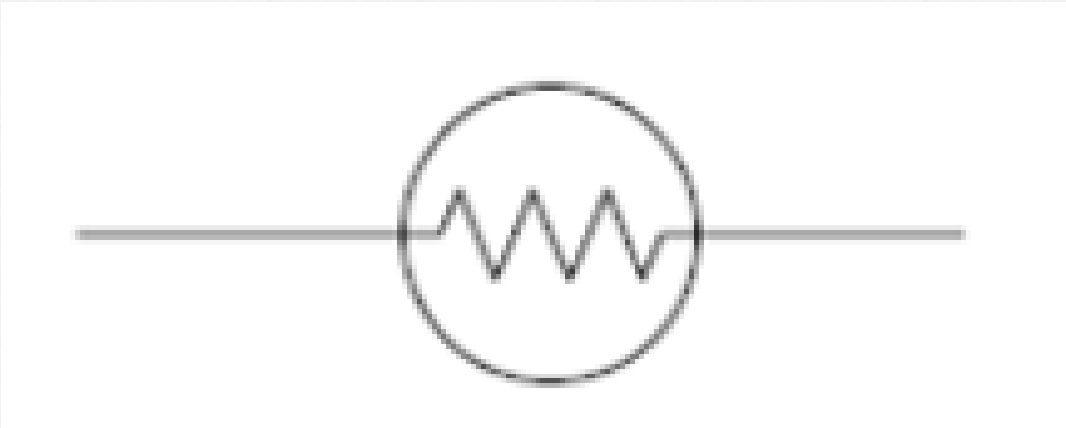




# SPST switch

Single Pole Single Throw

Pole is moving part in middle

Throw is a place for the pole to connect

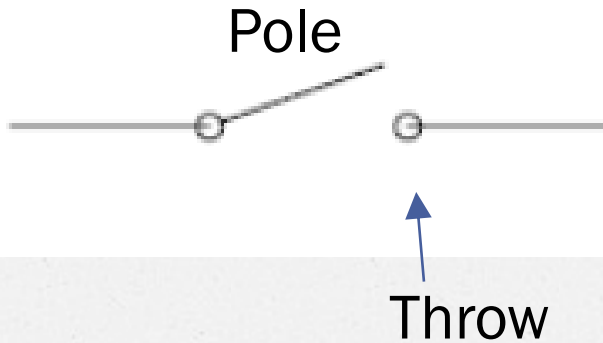

Used for simple  
ON/OFF switch

# HOMework! :)

Make sure to:

Memorize flashcards

Build more circuits (start with the ones in this slideshow then be creative and build your own)

Check out these cool videos/apps:

[Link #1](#) – BBC app on circuit basics

[Link #2](#) – PBS video on circuit basics

[Link #3](#) – B is for Battery video

[Link #4](#) – A is for Ampere video

[Link #5](#) – Circuit Builder (fairly advanced, it will make more sense after each workshop)