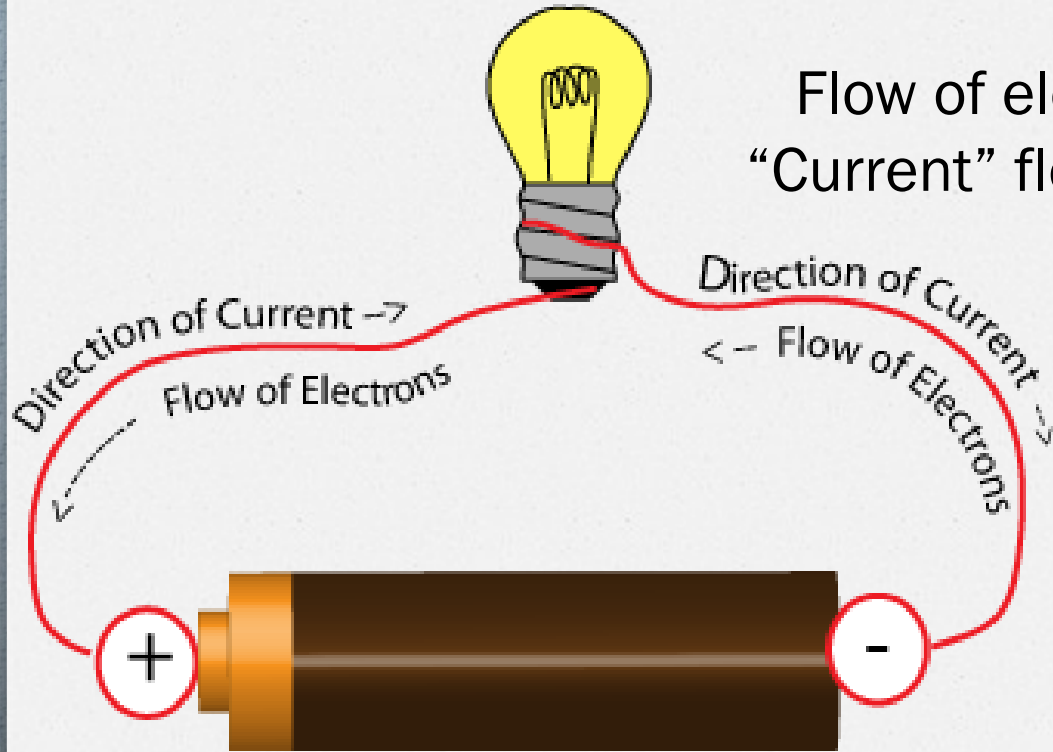


# Circuit Wizardry Workshop #2

Presented by:  
Optics Society at the University of Michigan

# Current



Flow of electrons (like a river)  
“Current” flows from (+) side of  
battery to (-) side

Electrons go the  
other way

# Conductor

Allows easy flow of electrons




Examples: Copper wire(shown in picture), paper clip, any metal  
Skin is a “weak” conductor


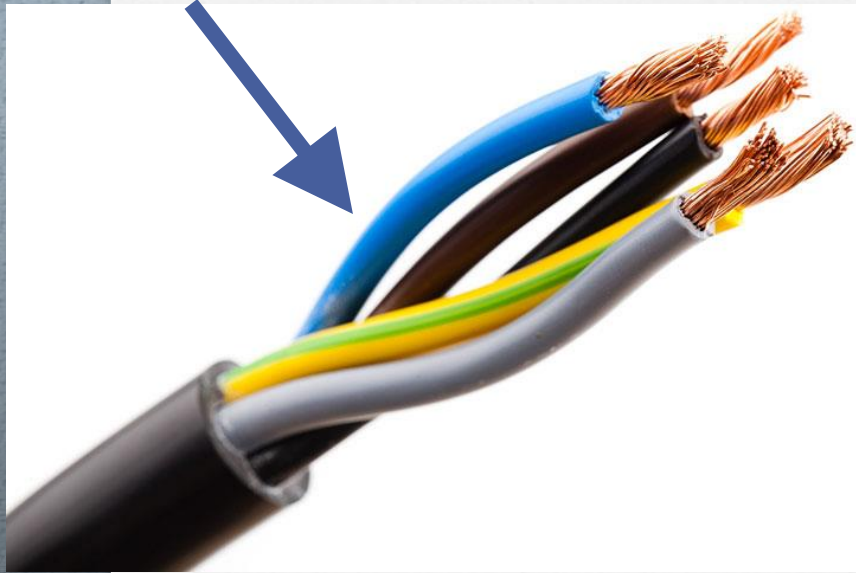
# Insulator



Does NOT allow electrons to flow at all. (No conduction)




Examples: Rubber (shown in picture), wood, cloth, plastic, cardboard


# Voltage

Voltage is like pressure (sort of)

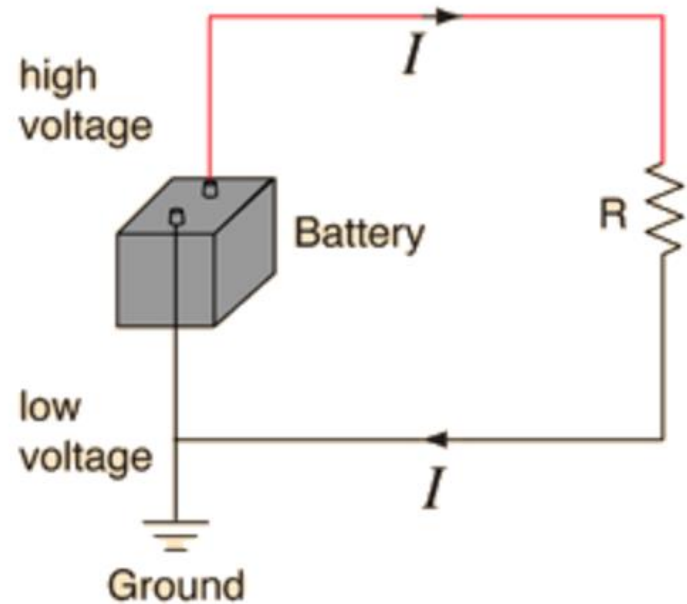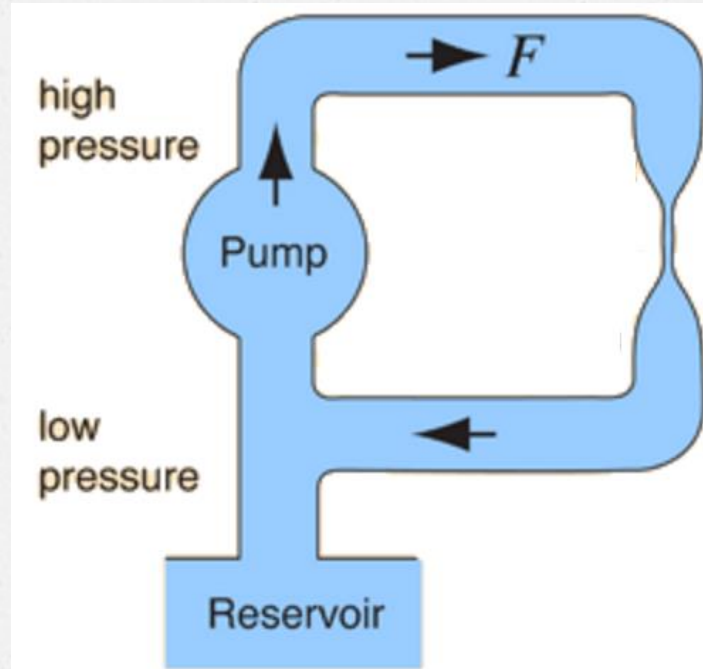


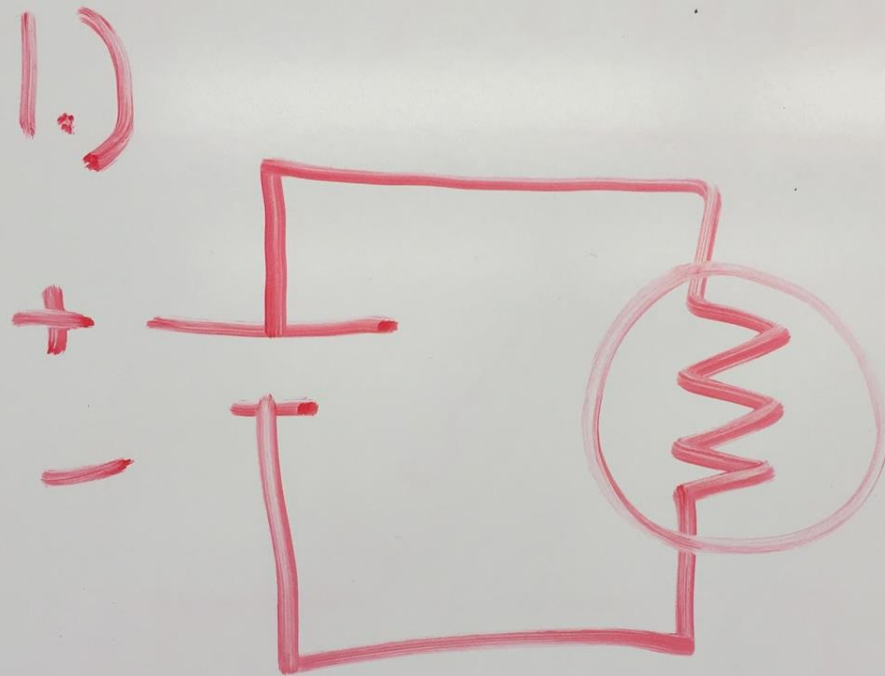



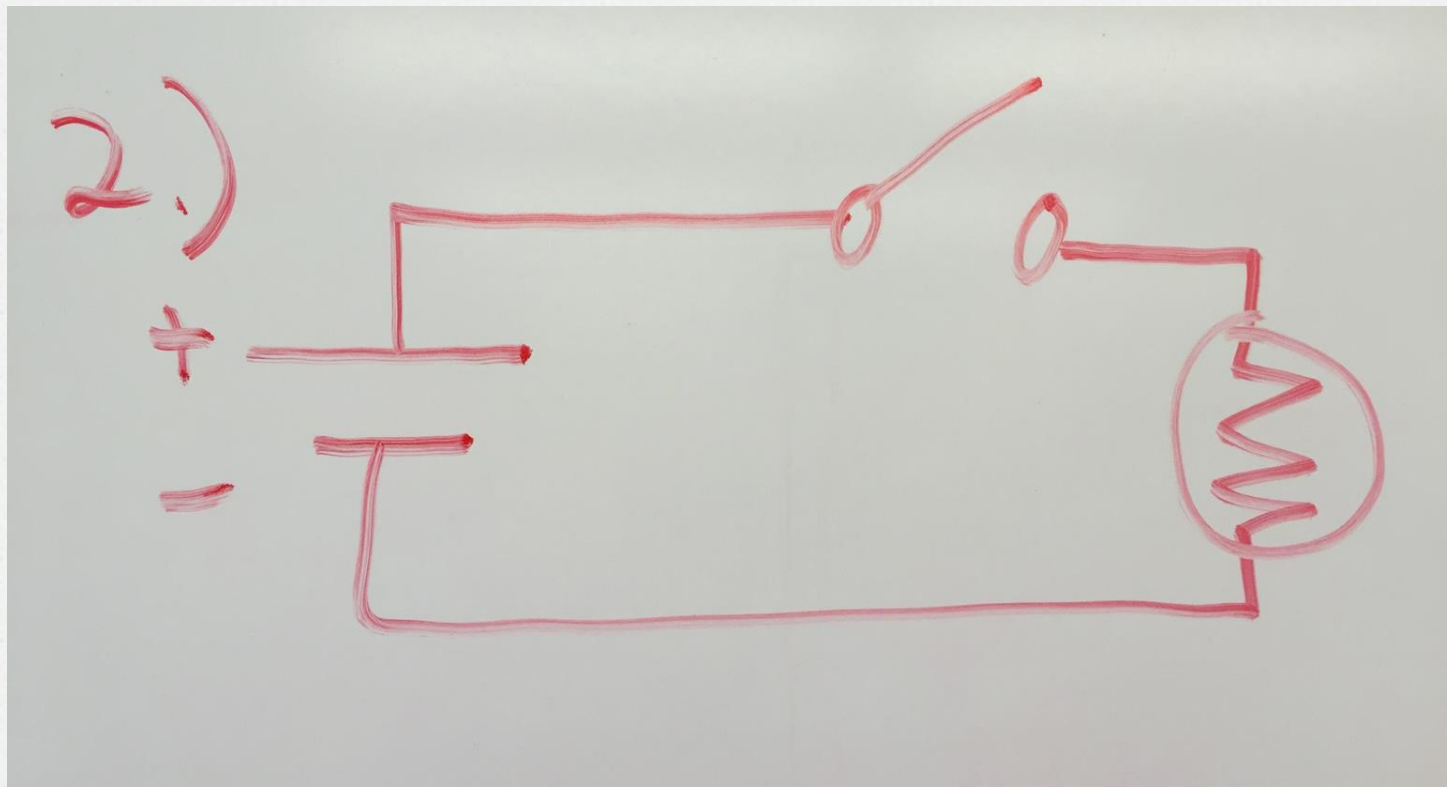



3.)

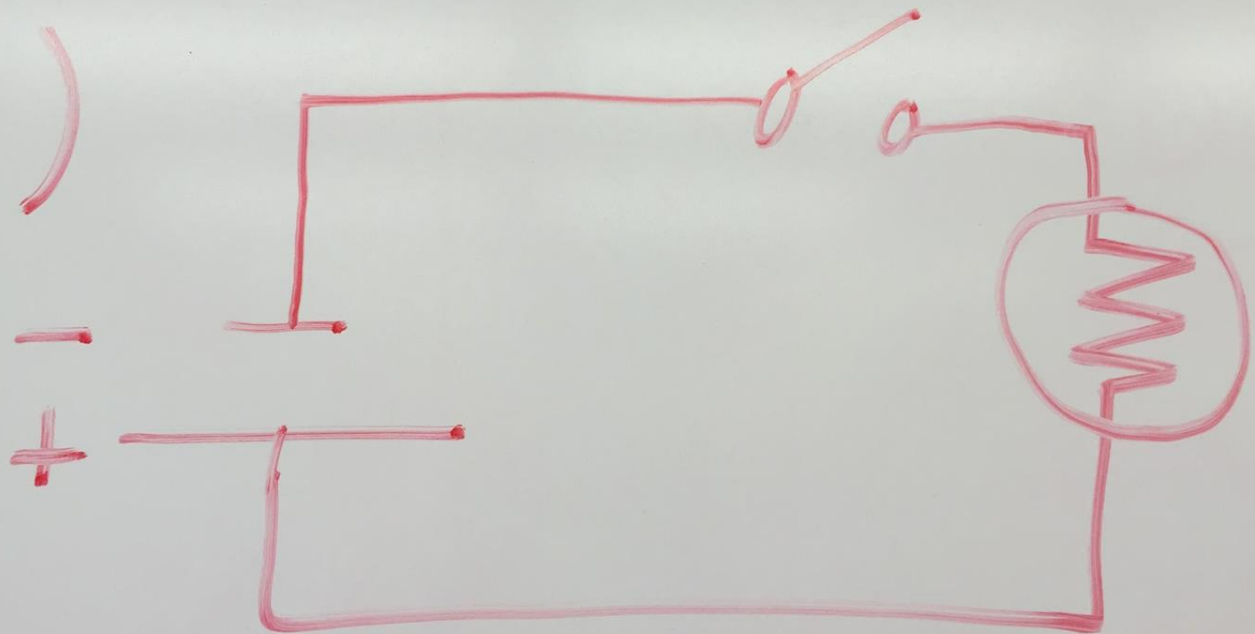



4.)

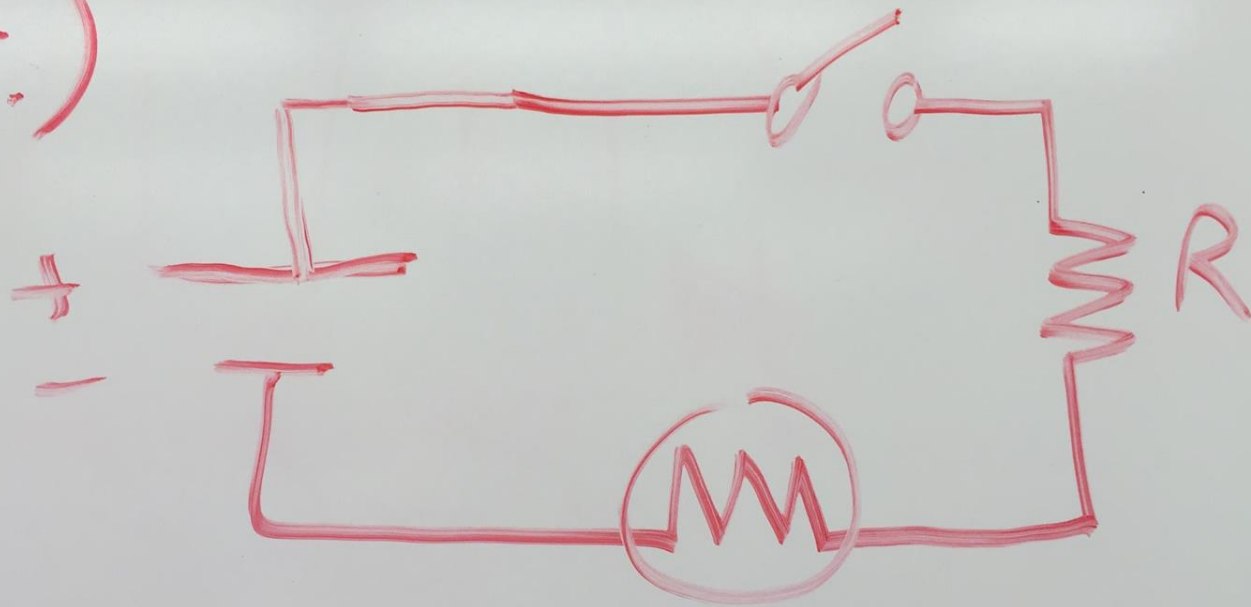

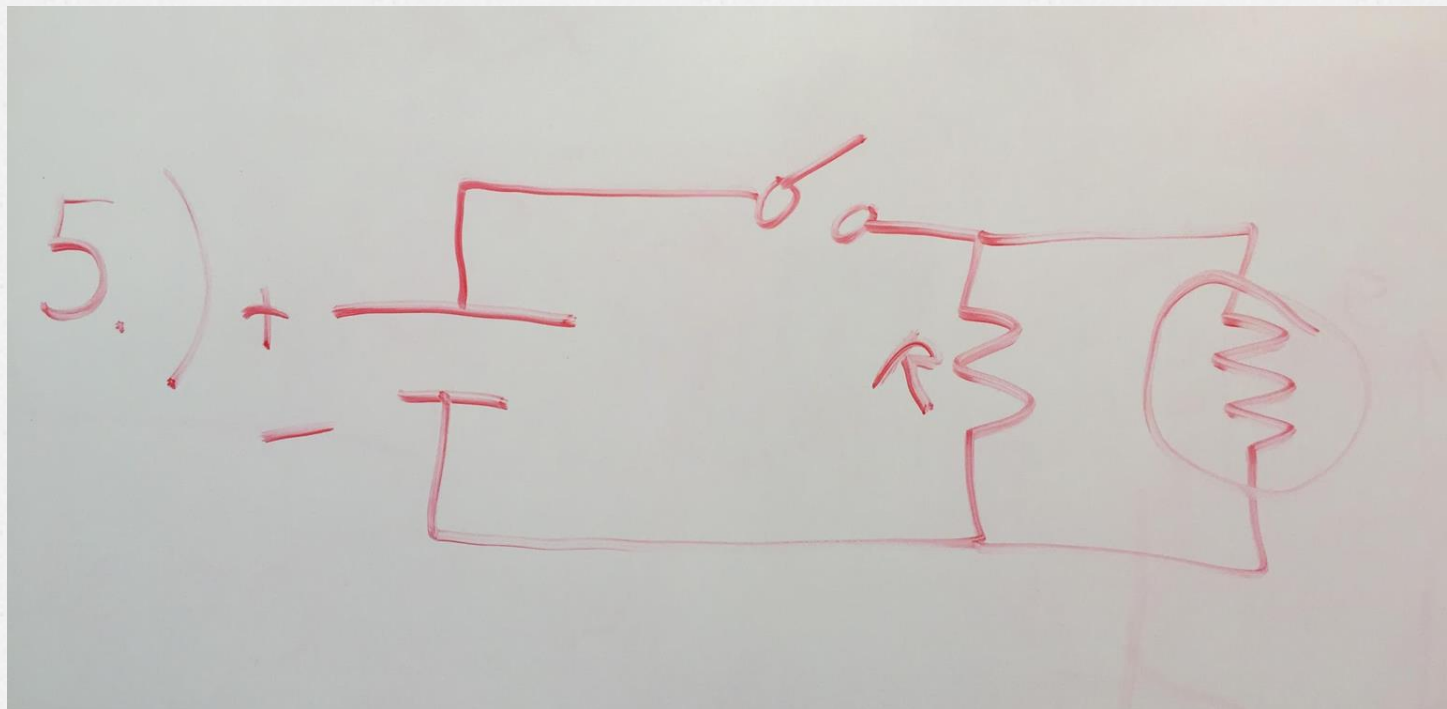




# Series & Parallel




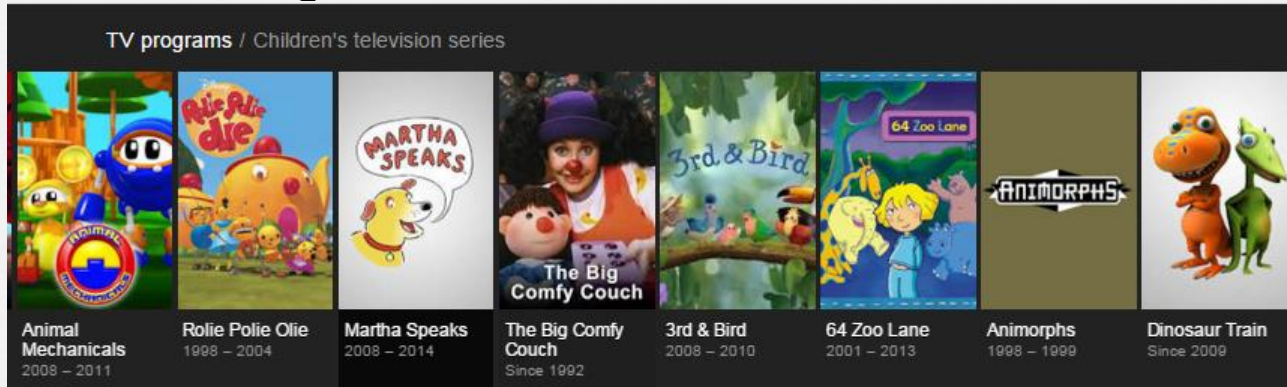
# What do you think of when you hear *series*?




- Like episodes, things in series all go in a line

# Series

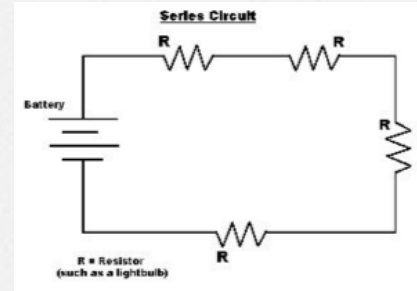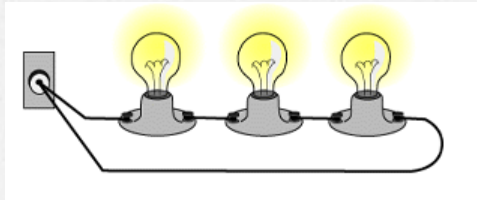



- Light bulbs can be in series, resistors can be in series, batteries can be in series...
- How many things are in series in these pictures?

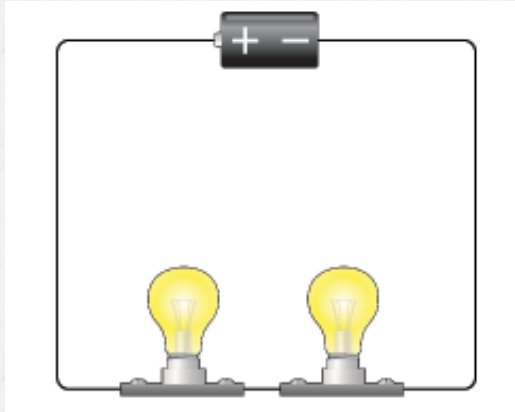What happens if a bulb breaks  
in *series*?




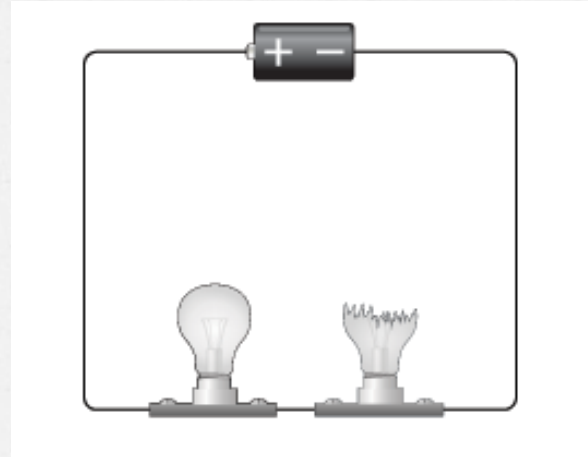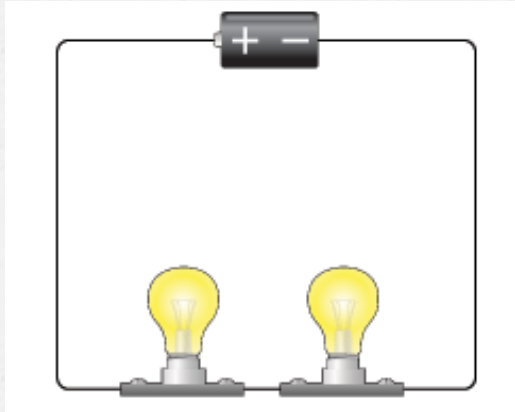
# What happens if a bulb breaks in *series*?





What do you think of when  
you hear *parallel*?



- Parallel bars, parallel lines

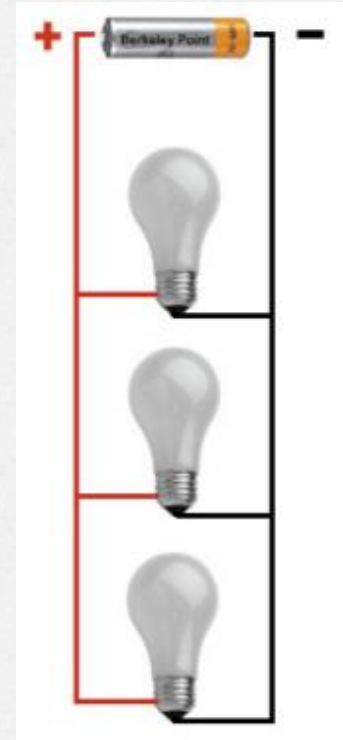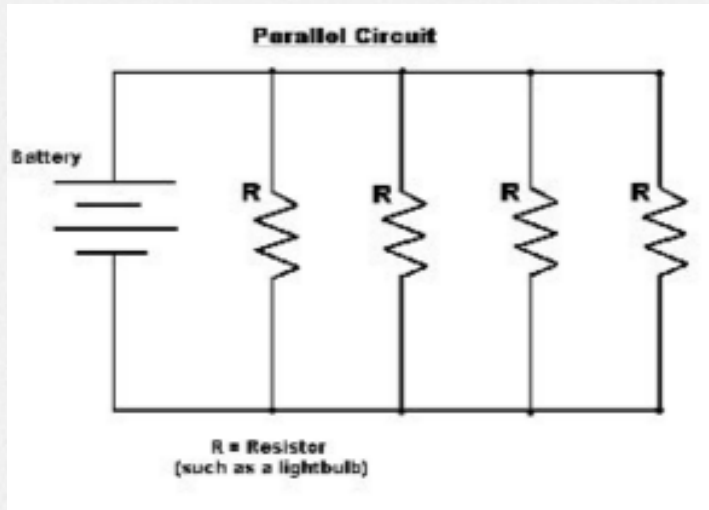
# Parallel

- Parallel circuits often look like several boxes, or a ladder.







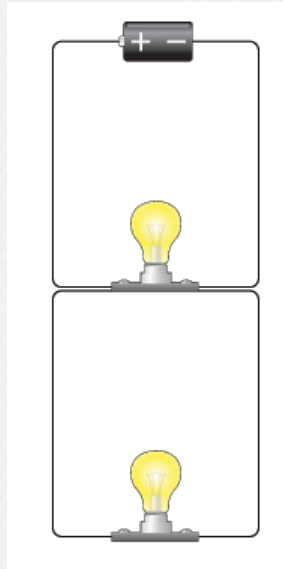What happens if a bulb breaks  
in *parallel*?



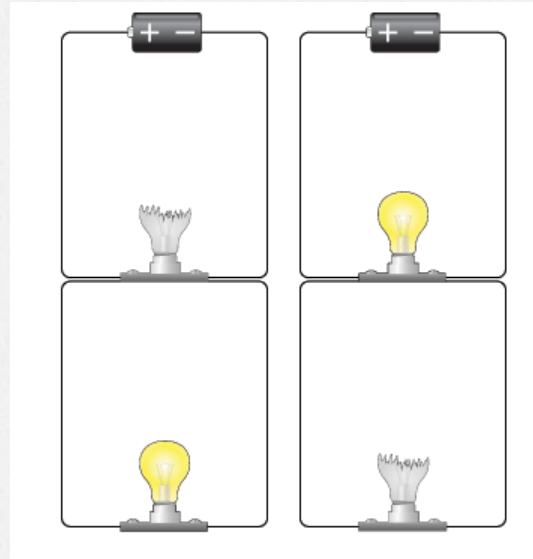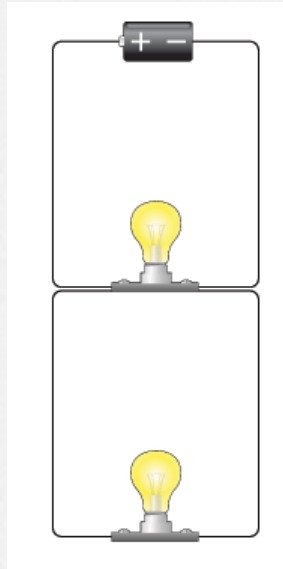
# What happens if a bulb breaks in *parallel*?



# Current
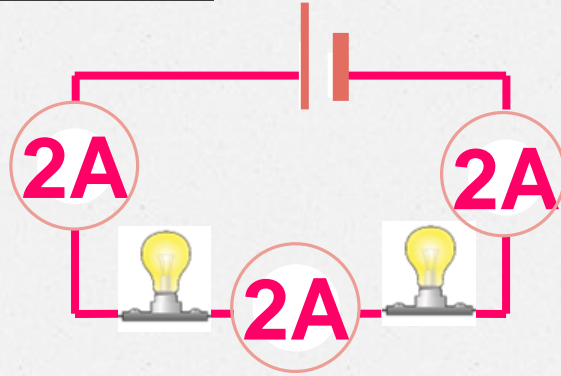
## SERIES CIRCUIT

- current is the same at all points in the circuit.






# Current

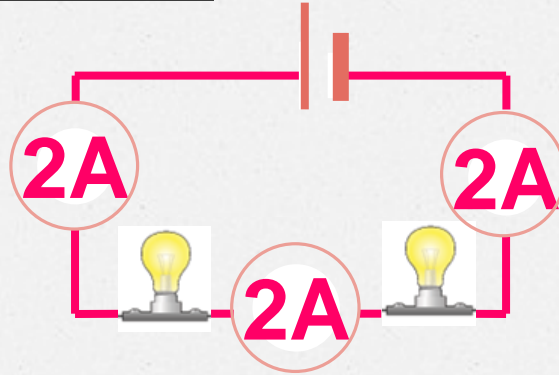
## SERIES CIRCUIT

- current is the same at all points in the circuit.



## PARALLEL CIRCUIT


- current is split between each branch

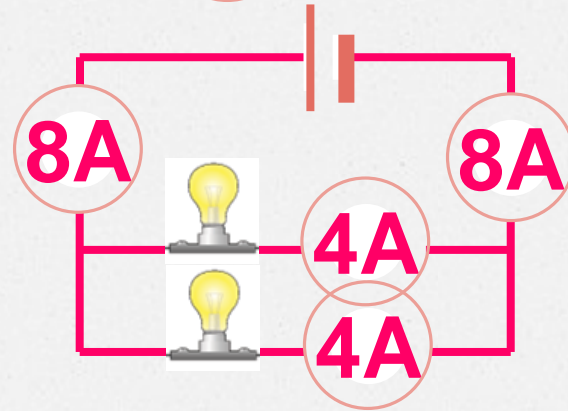

# Voltage

## SERIES CIRCUIT


- voltage is the split across components

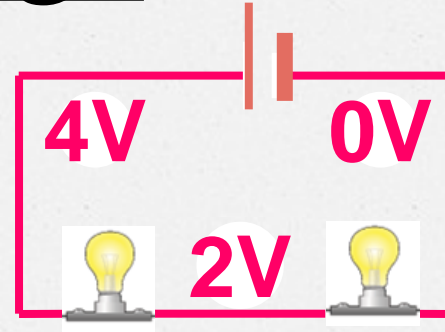

# Voltage


## SERIES CIRCUIT

- voltage is the split across components

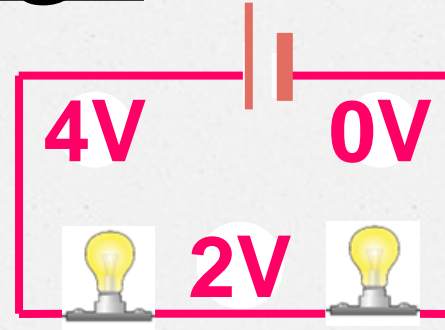

## PARALLEL CIRCUIT


- voltage is same across each branch

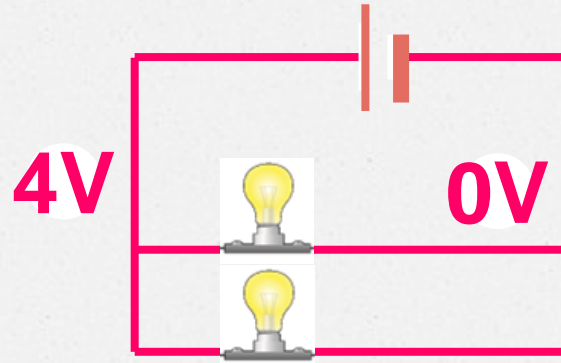



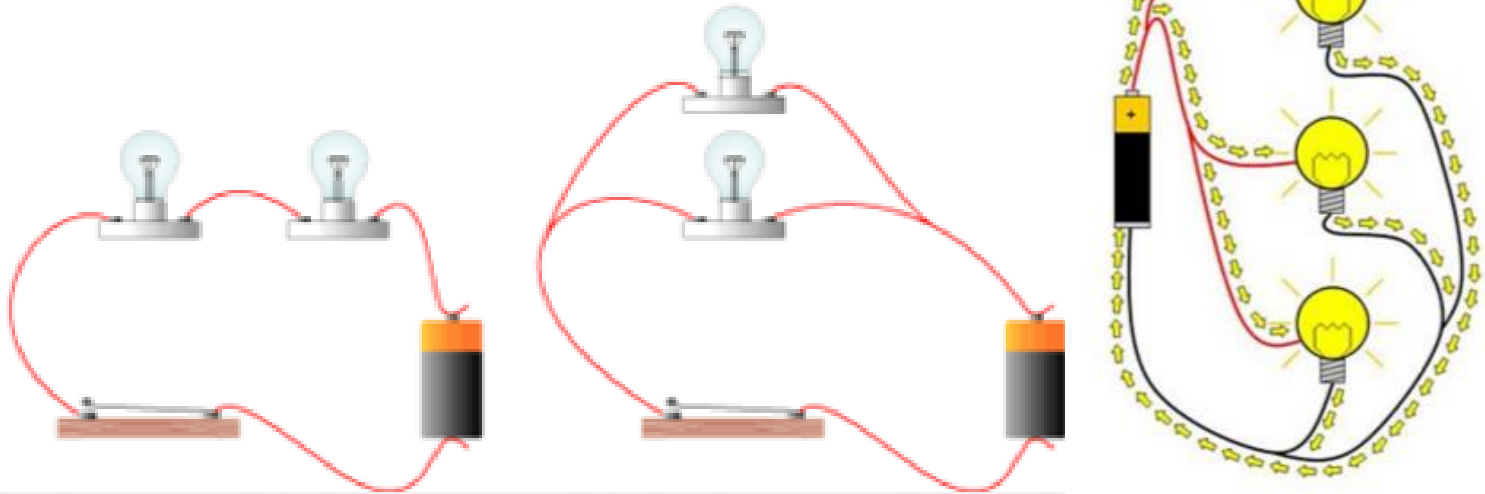
# Series and Parallel

- Remember, things in series, will be in a continuous loop, where things in parallel will be in their own loop









What is in series?

What is parallel?

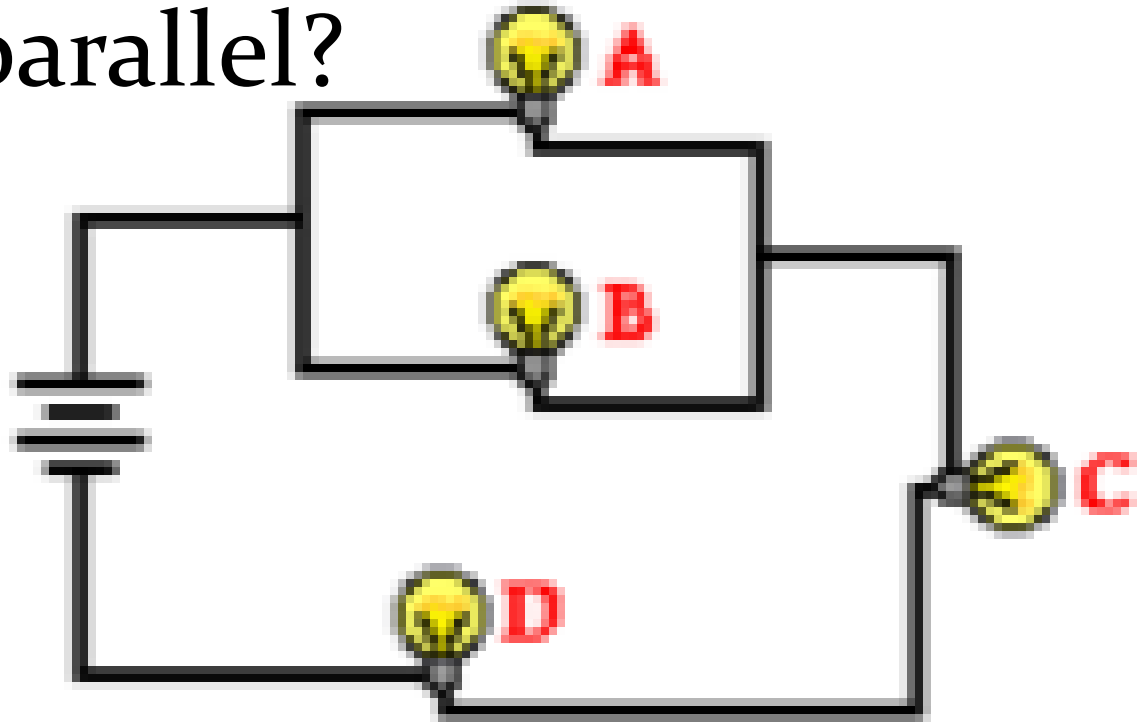

Series,  
Parallel,  
or both?

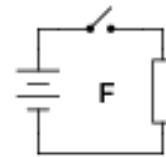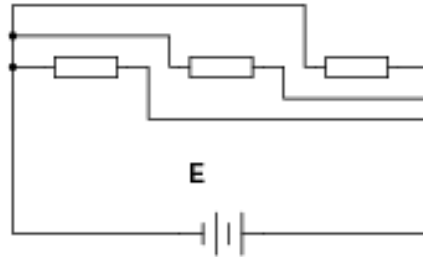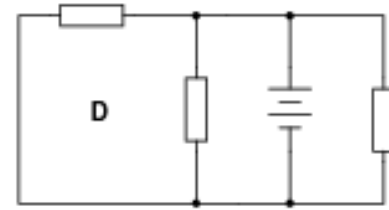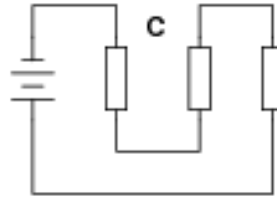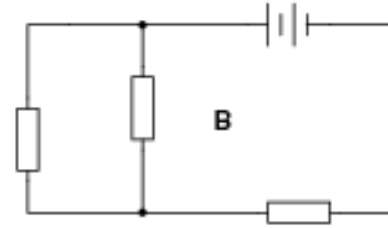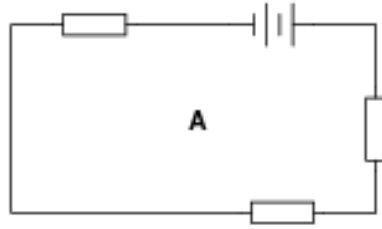



# Let's Compare Series and Parallel Circuits

## Series Circuits

o 1 path(s) for current

## Parallel Circuits

o multiple path(s) for current

# Let's Compare Series and Parallel Circuits

## Series Circuits

- o 1 path(s) for current
- o Current is the same at every point

## Parallel Circuits

- o multiple path(s) for current
- o Current can be different in each branch

# Let's Compare Series and Parallel Circuits

## Series Circuits

- o 1 path(s) for current
- o Current is the same at every point
- o Voltage drops at each resistor

## Parallel Circuits

- o multiple path(s) for current
- o Current can be different in each branch
- o Voltage same across each resistor



# Let's Compare Series and Parallel Circuits

## Series Circuits

- o 1 path(s) for current
- o Current is the same at every point
- o Voltage drops at each resistor
- o Break in circuit stops all current

## Parallel Circuits

- o multiple path(s) for current
- o Current can be different in each branch
- o Voltage same across each resistor
- o Break in circuit does not affect other bulbs

# Let's Compare Series and Parallel Circuits

## Series Circuits

- o 1 path(s) for current
- o Current is the same at every point
- o Voltage drops at each resistor
- o Break in circuit stops all current
- o Adding resistance in series decreases total current (dimmer light bulbs)

## Parallel Circuits

- o multiple path(s) for current
- o Current can be different in each branch
- o Voltage same across each resistor
- o Break in circuit does not affect other bulbs
- o Adding resistance in parallel increases total current



More Switches!



# SPDT switch



OR



Single Pole Double Throw

One pole in the middle


It has two options for  
where to connect  
(double throw)

# DPST switch

Double Pole Single Throw

TWO poles!

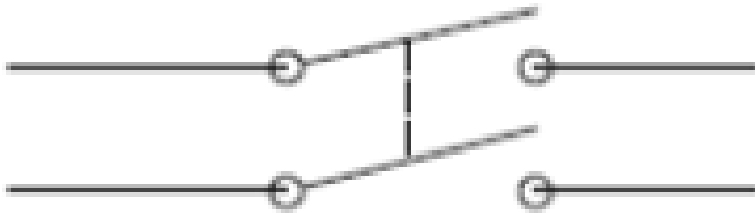But each pole only has  
place to go (single  
throw)




Looks like two SPST  
switches glued together

# DPDT switch

Double Pole Double Throw



OR

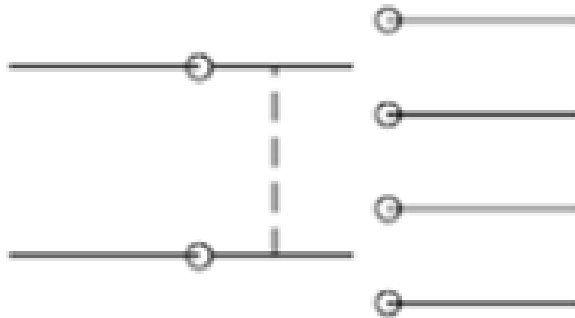

Two poles again


Each pole has TWO options for where to connect (double throw)


Looks like two SPDT switches glued together







Practice Practice Practice...

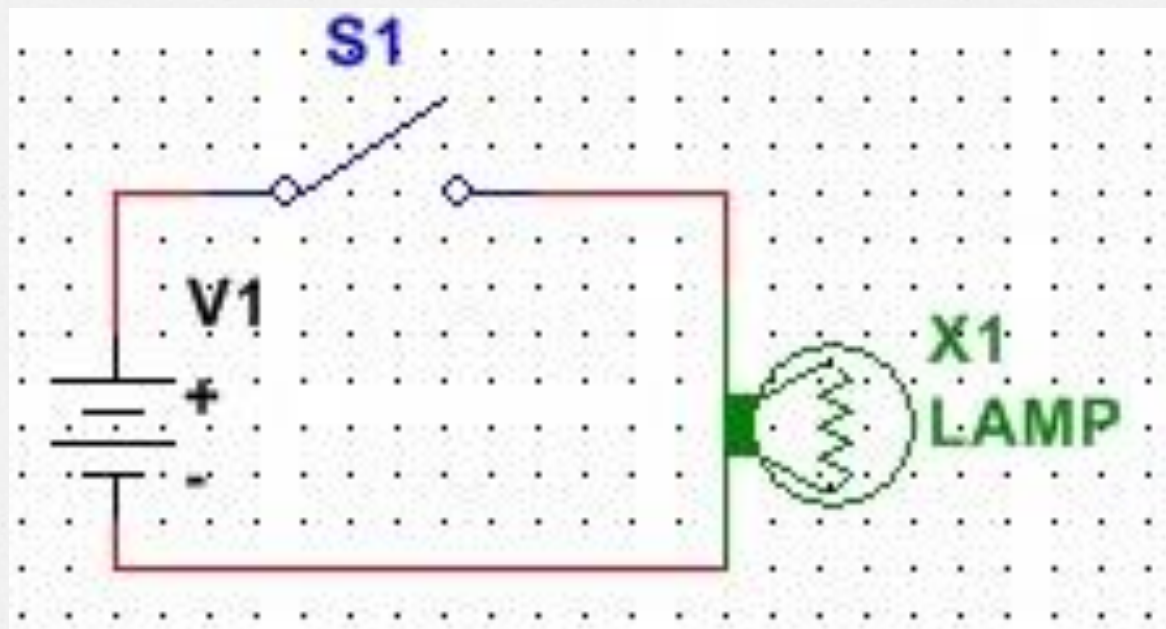

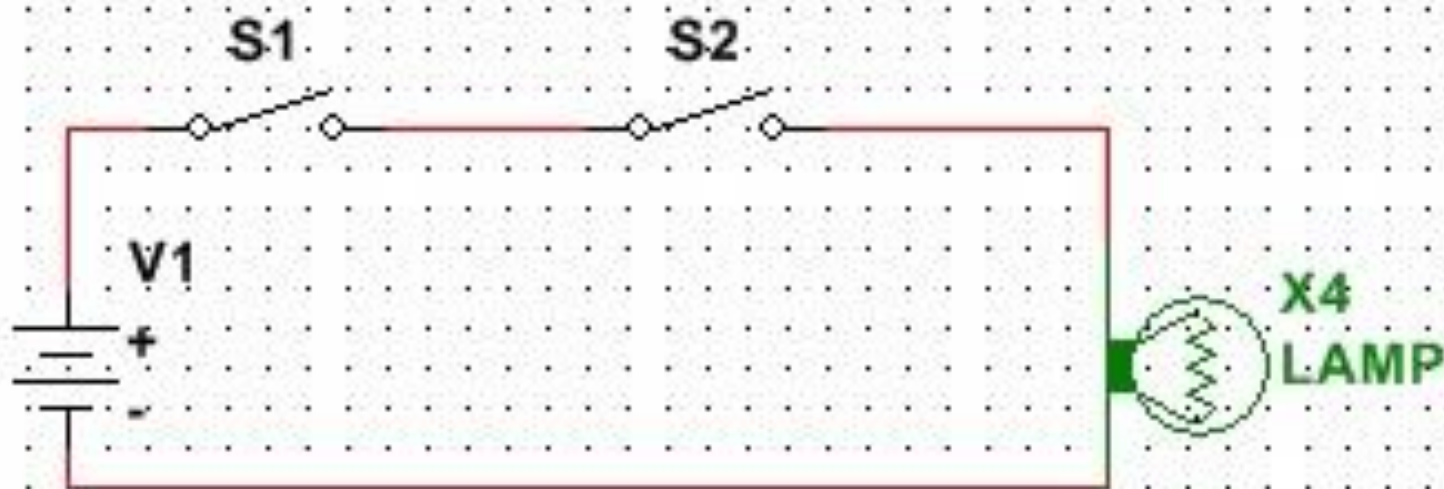




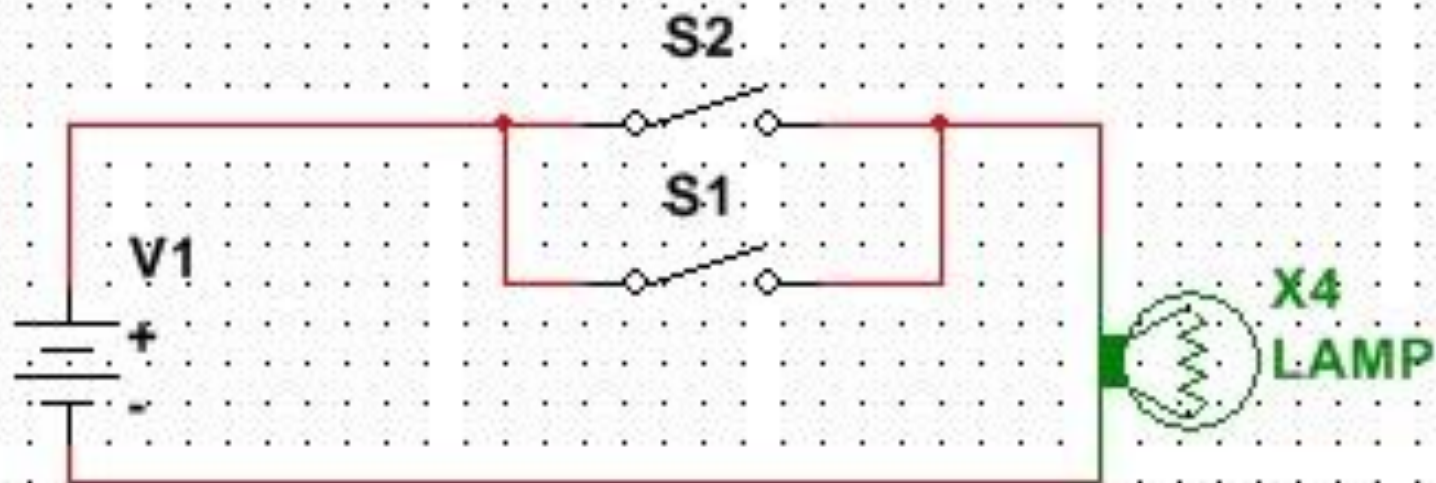


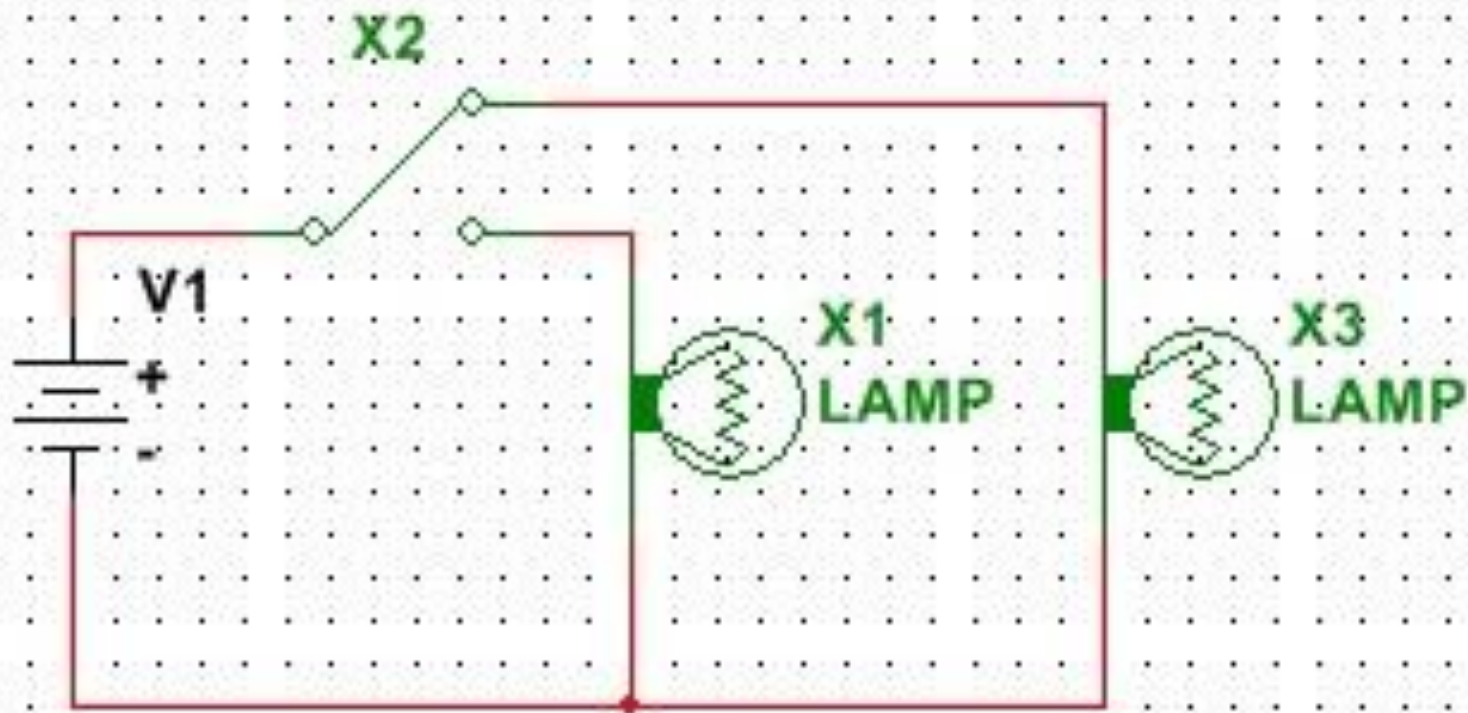




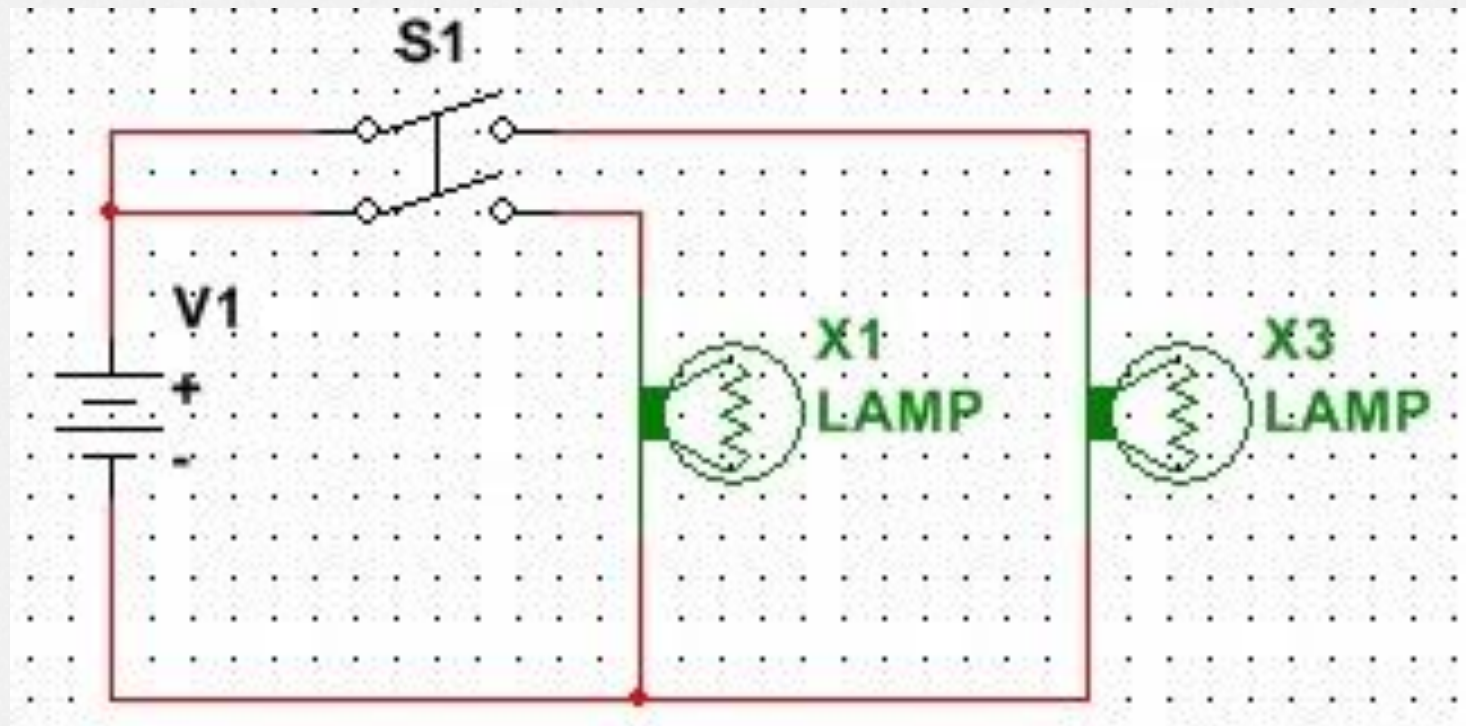




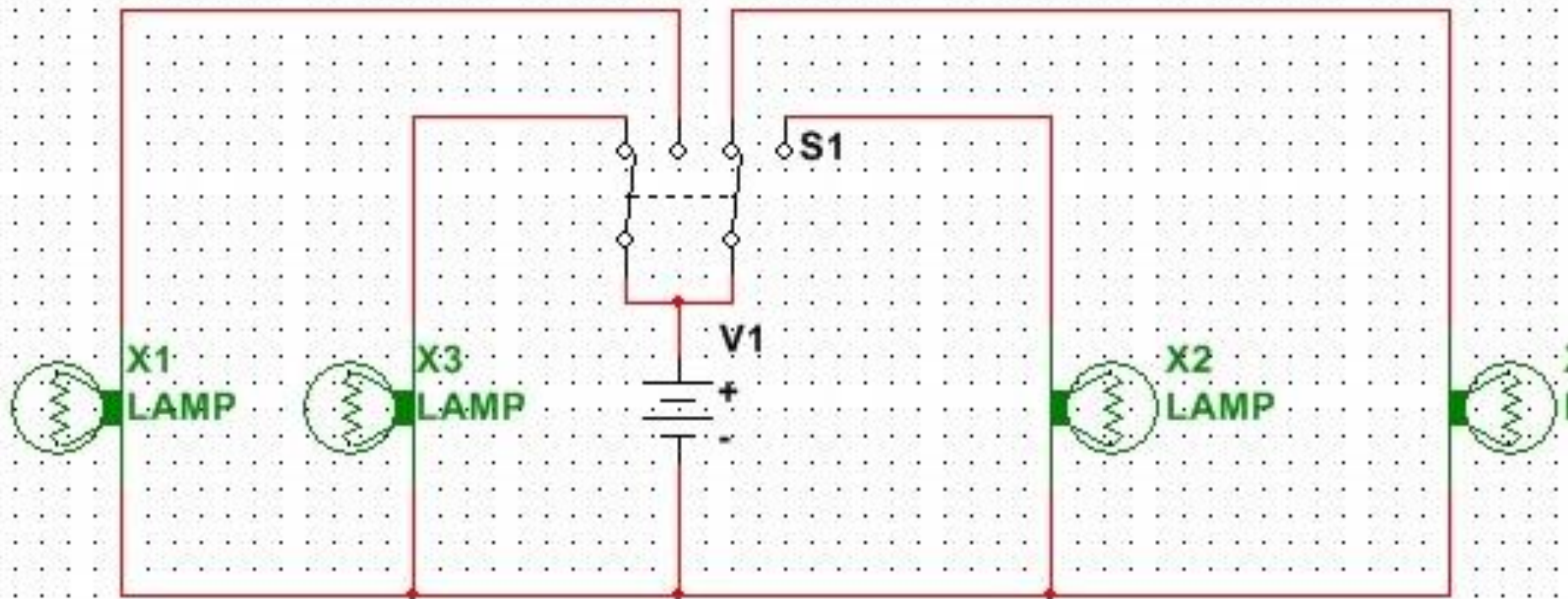

# Diodes and LEDs

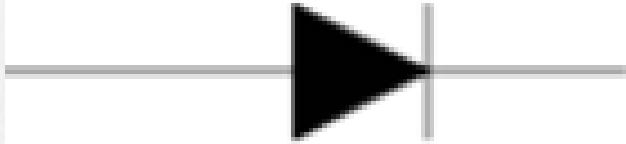


Current  

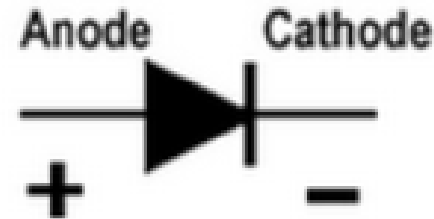  
Electrons


# ACID:

Anode  
Current  
Into  
Device



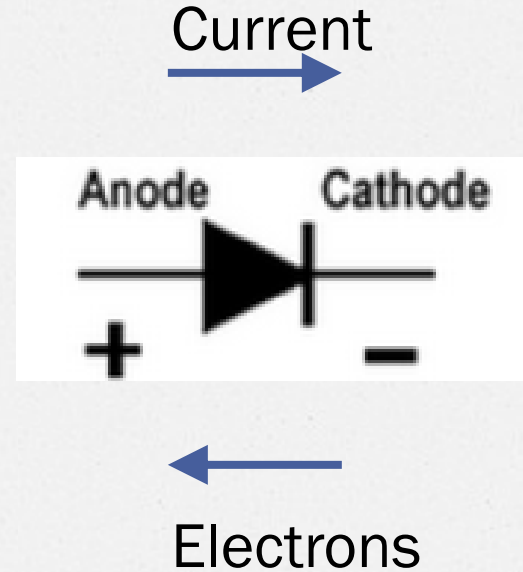




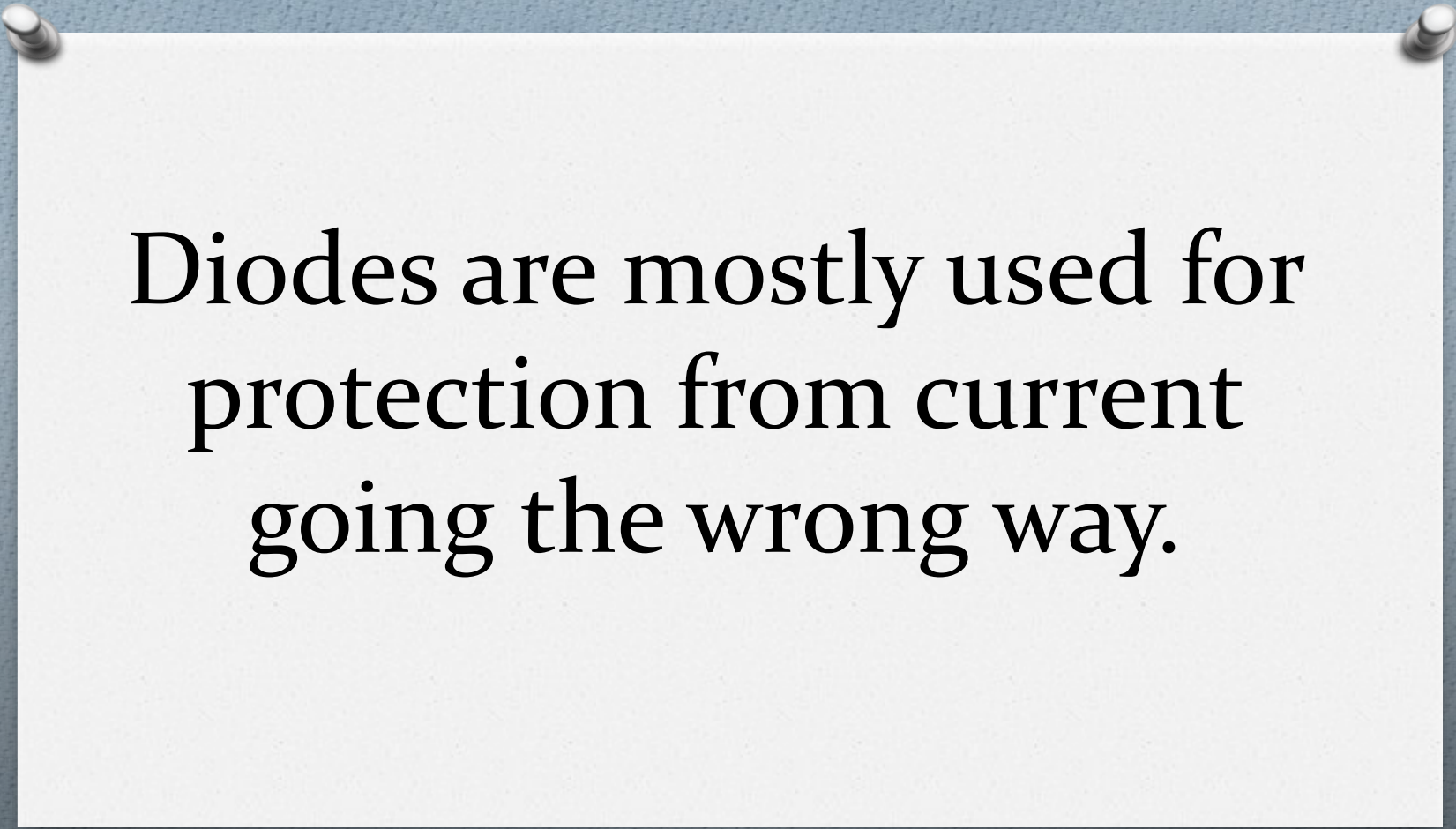



Diodes are mostly used for protection from current going the wrong way.
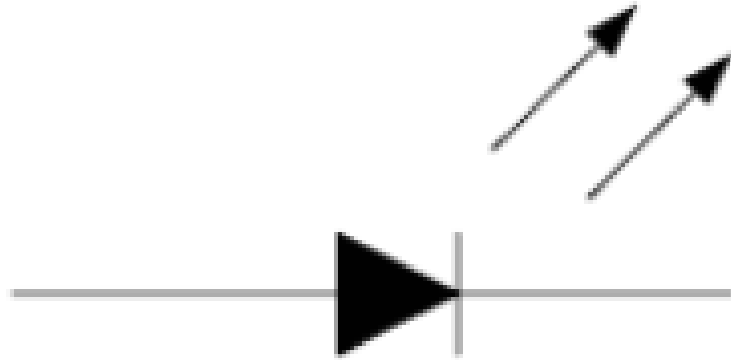
# Light Emitting Diode


Same as diode but also releases energy (as light)






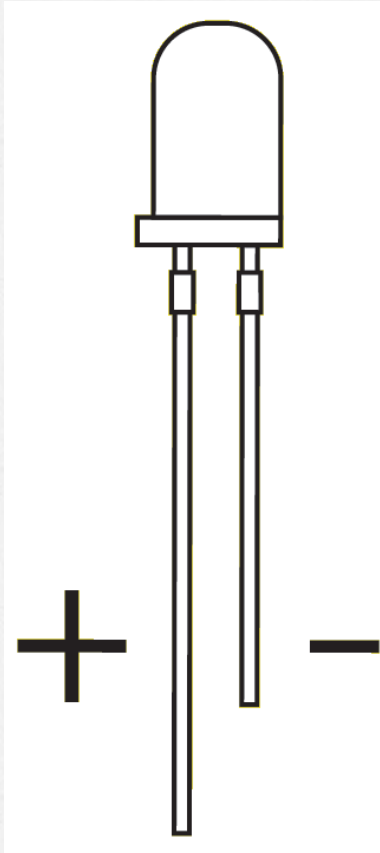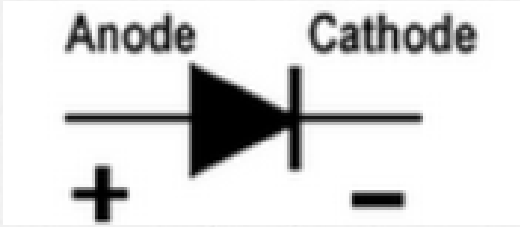


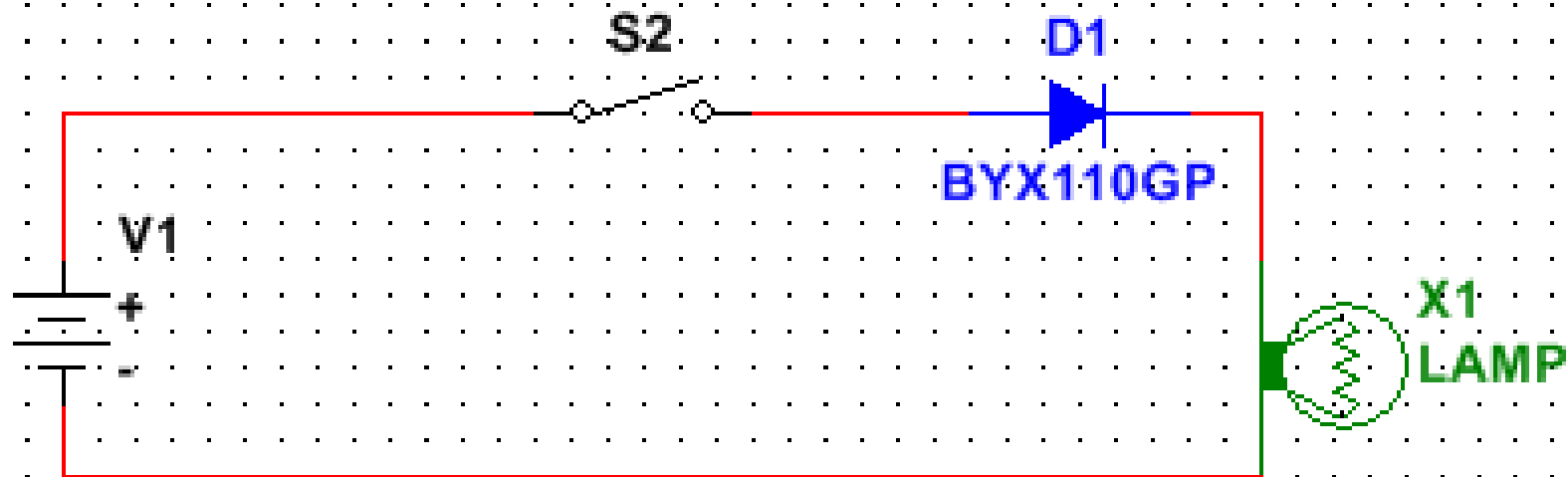
Just like battery,  
the (+) side is  
longer



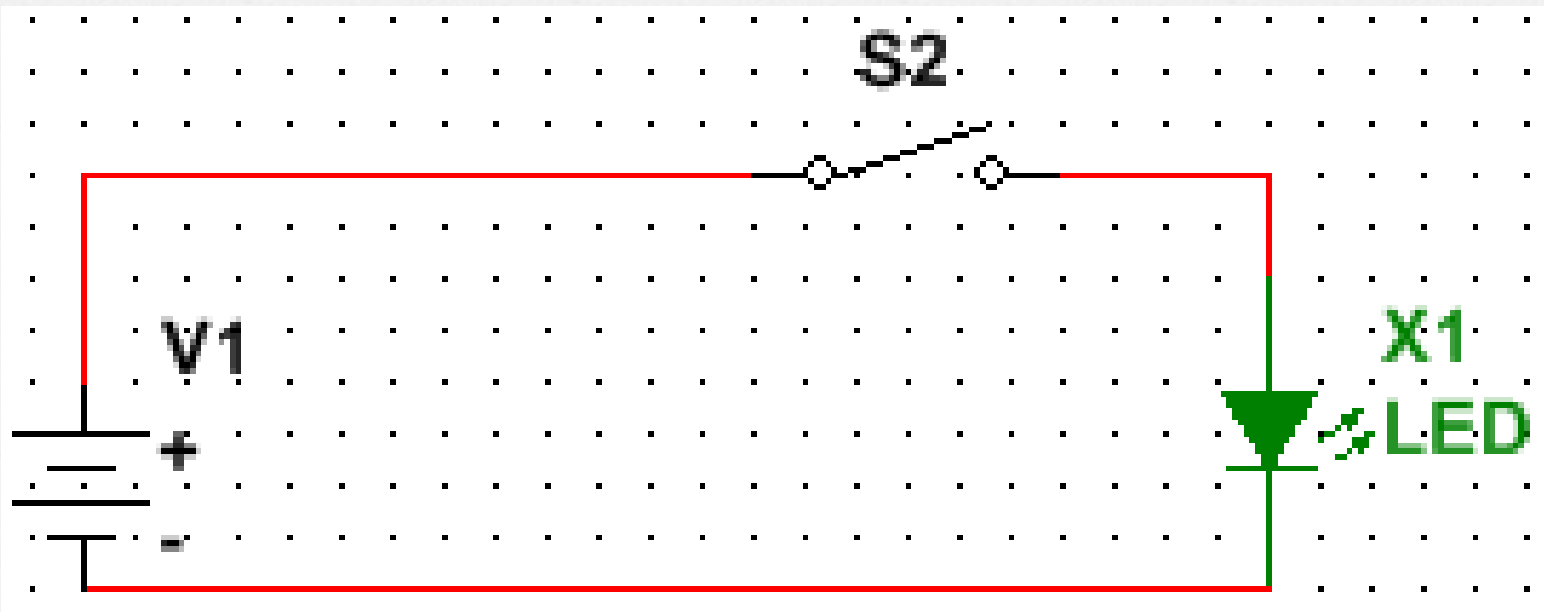



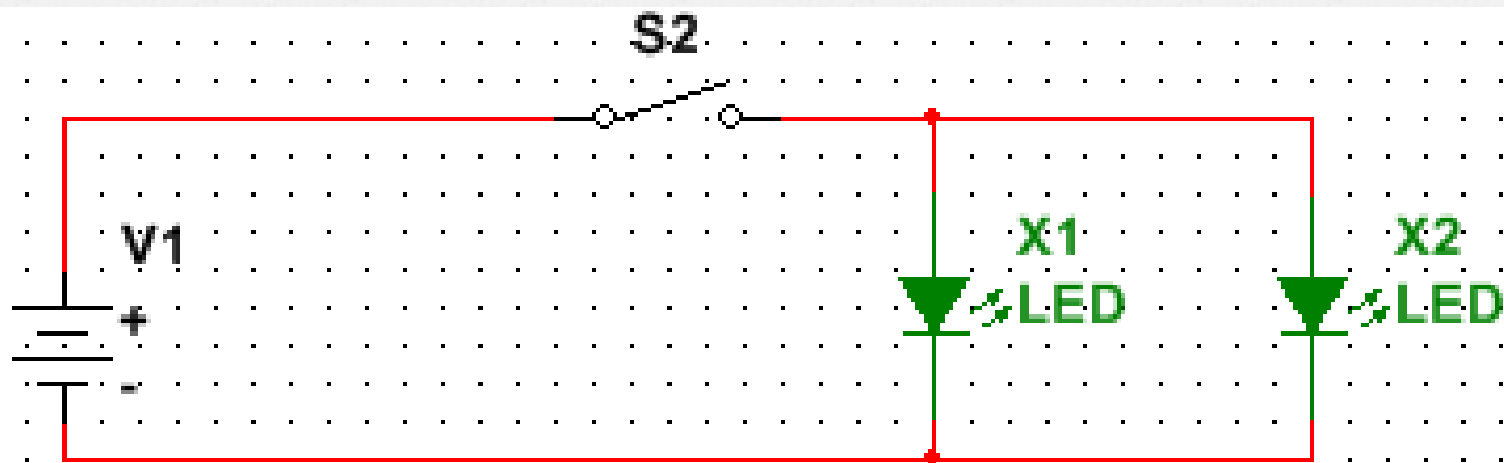

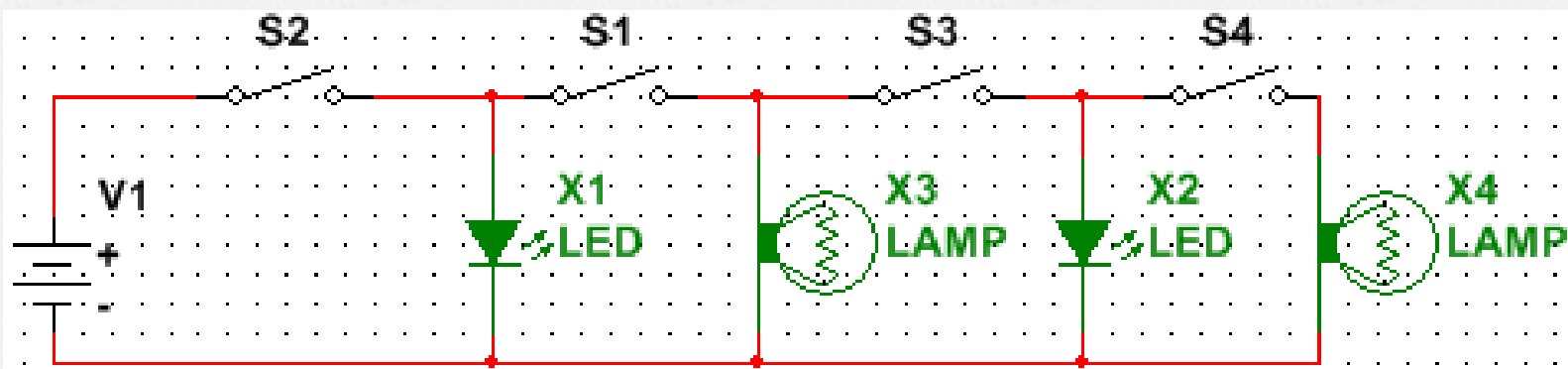



# Flashcards



# SPDT switch



OR



Single Pole Double Throw

One pole in the middle


It has two options for  
where to connect  
(double throw)

# DPST switch

Double Pole Single Throw

TWO poles!

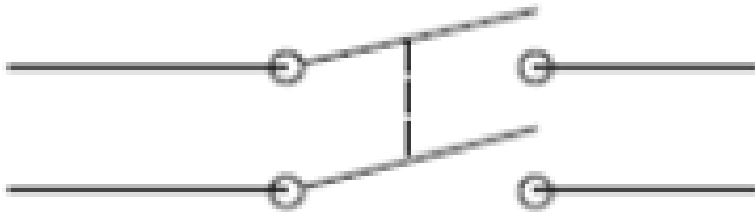But each pole only has  
place to go (single  
throw)




# DPDT switch

Double Pole Double Throw



OR

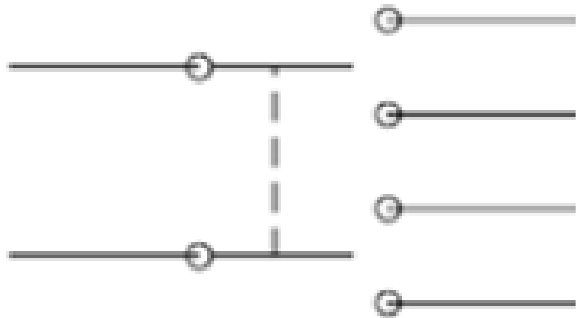


Two poles again

Each pole has TWO options for where to connect (double throw)




# Diode

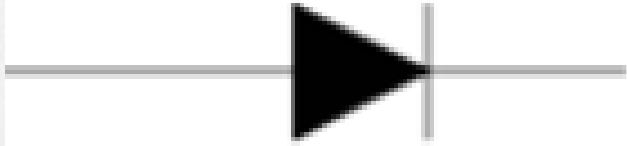

Only allows current in one direction (it's a one way street!)


Remember electrons go opposite way as current!

Current  

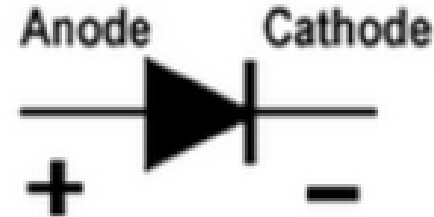  
Electrons

# LED

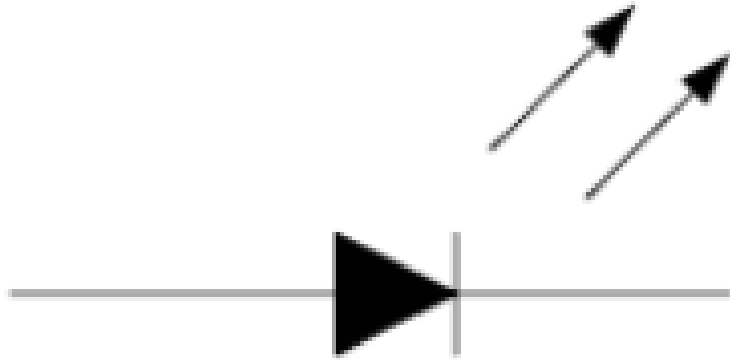

Light Emitting Diode

Same as diode but also  
releases energy (as  
light)

# To do at home :)

Make sure to:

Memorize flashcards

Build more circuits (start with the ones in this slideshow then be creative and build your own)

Check out these cool videos/apps:

[Link #1](#) – Series and Parallel Circuit Builder (really helpful!)

[Link #2](#) – D is for Diode

[Link #3](#) – Another Circuit Builder (this one shows voltage and current)

[Link #4](#) – Falstad Circuit Builder (fairly advanced, it will make more sense after each workshop)

[Link #5](#) – Switch tutorial (Sparkfun is a great website)