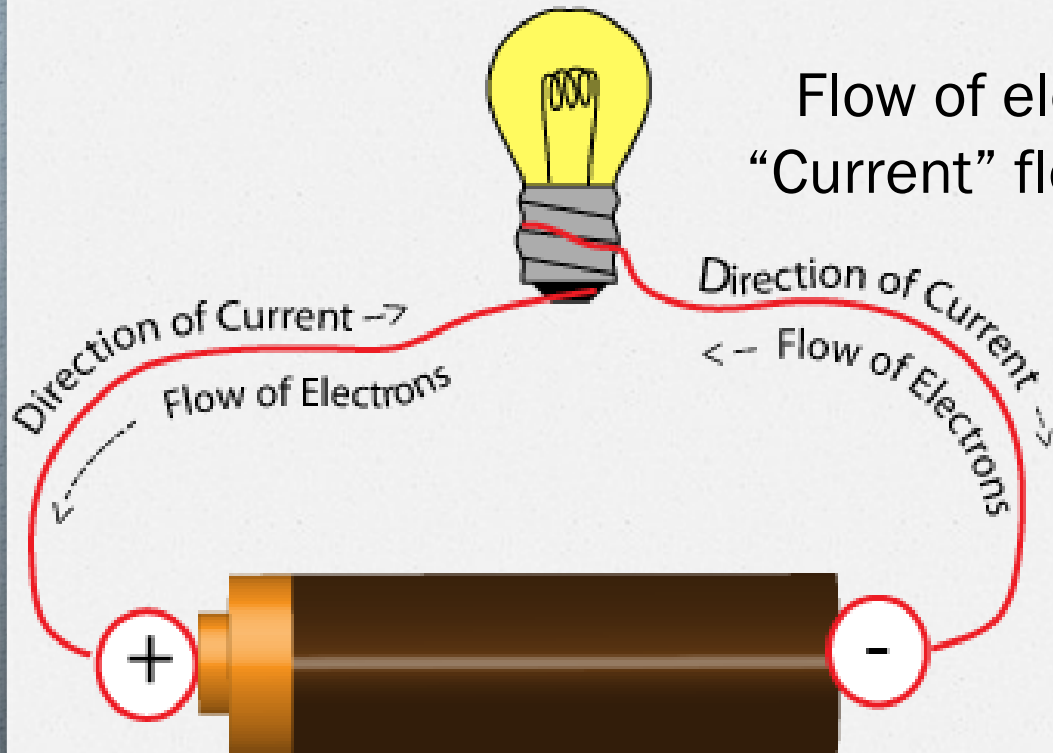


Circuit Wizardry Workshop #3

Presented by:
Optics Society at the University of Michigan

Current





Flow of electrons (like a river)
“Current” flows from (+) side of
battery to (-) side

Electrons go the
other way

Voltage


Voltage is like pressure (sort of)

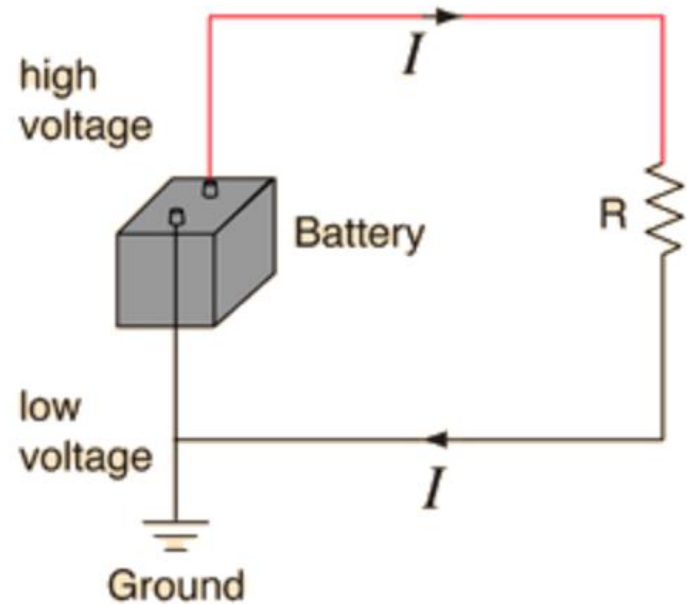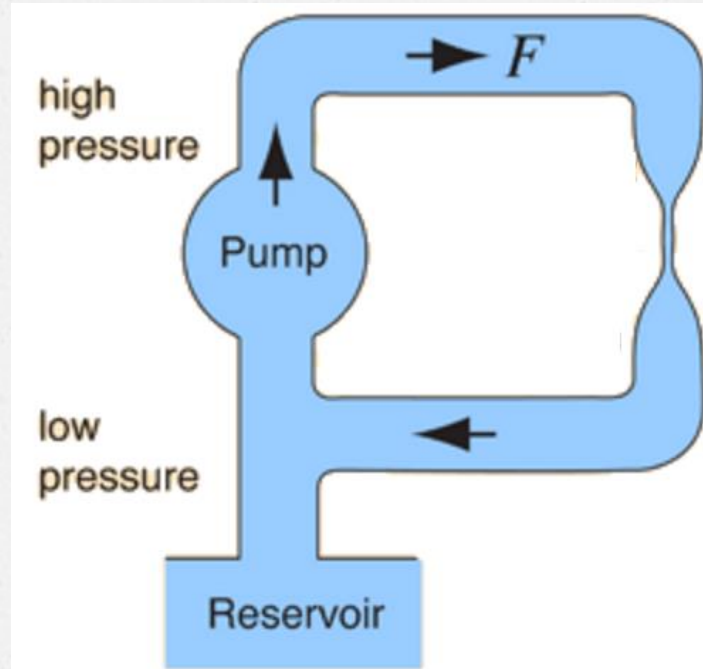

How to tell parallel & series?

Two components are in parallel if:

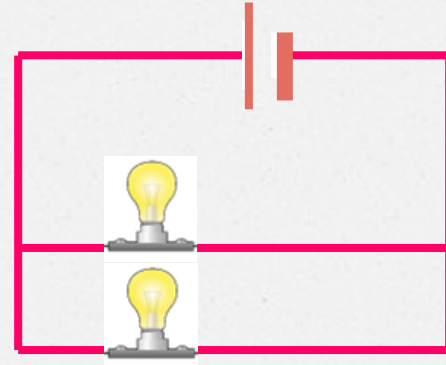Same sides of each component are both connected together with wires




(front to front AND back to back)

How to tell parallel & series?

Two components are in **series** if:


At least one set of opposite sides of each component are connected DIRECTLY together with a wire

(front to back OR back to front)

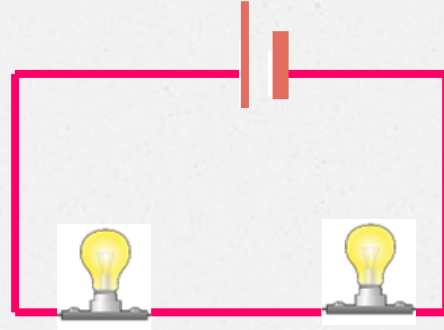

What is in series?


What is parallel?

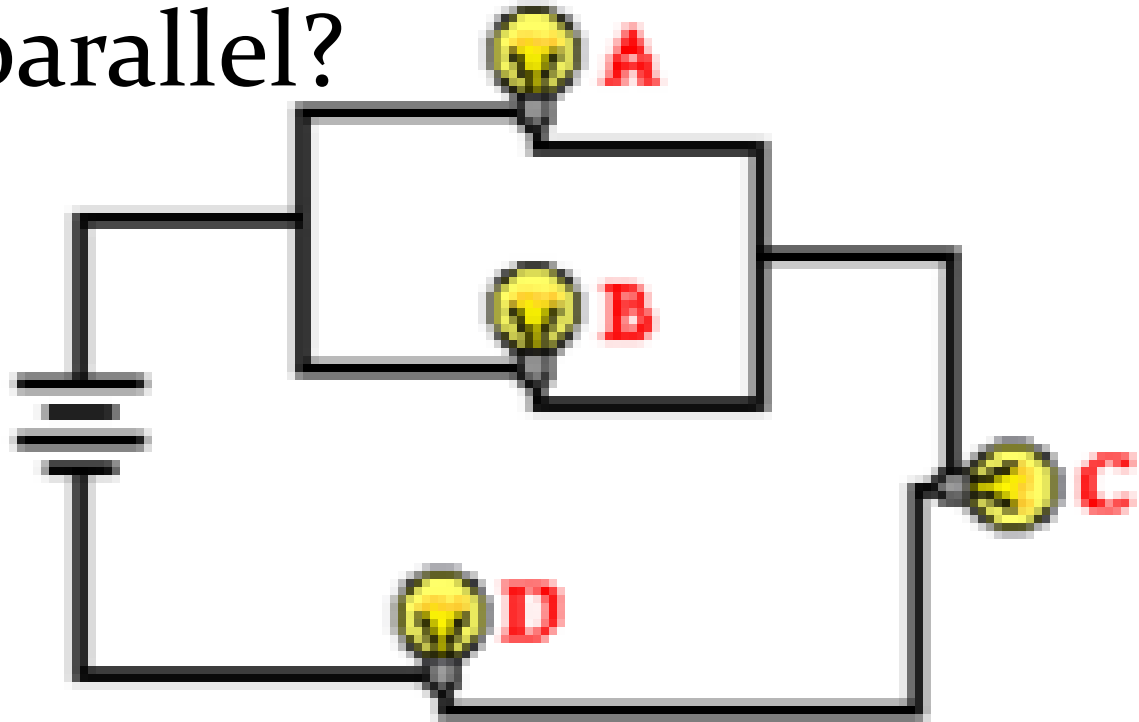

Current

SERIES CIRCUIT

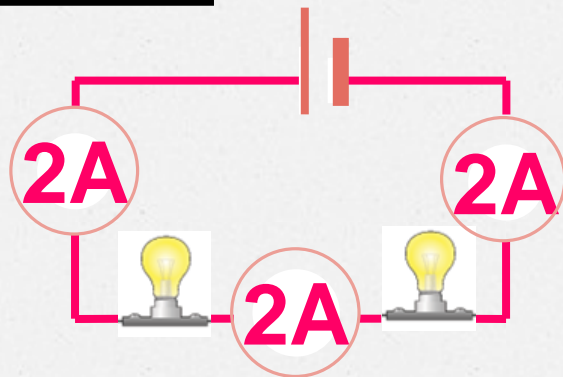
- current is the same at all points in the circuit.



Current


SERIES CIRCUIT

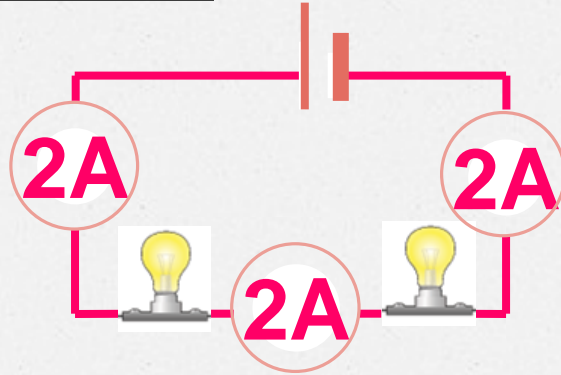- current is the same at all points in the circuit.



PARALLEL CIRCUIT


- current is split between each branch

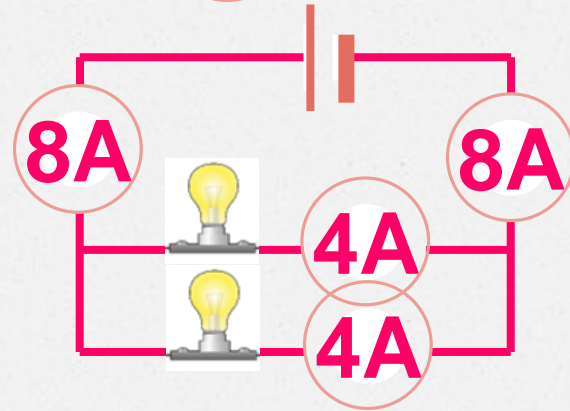

Voltage

SERIES CIRCUIT


- voltage is the split across components

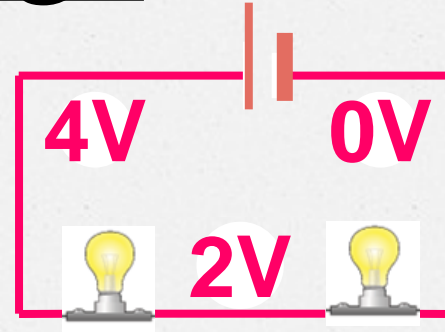

Voltage


SERIES CIRCUIT

- voltage is the split across components

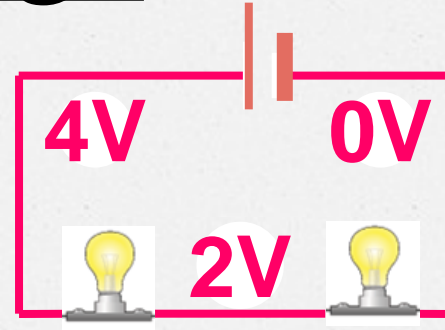


PARALLEL CIRCUIT


- voltage is same across each branch

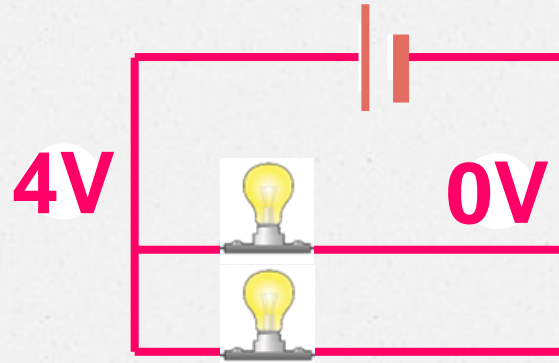

Diodes and LEDs

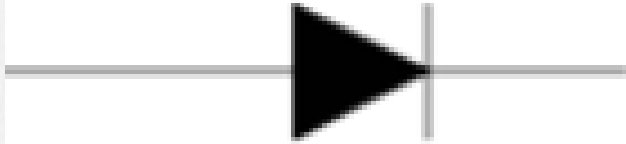


Current

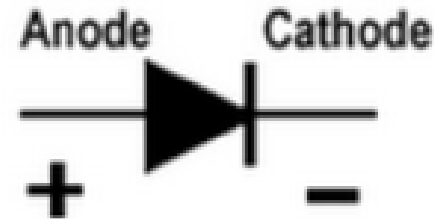
Electrons

ACID:


Anode
Current
Into
Device





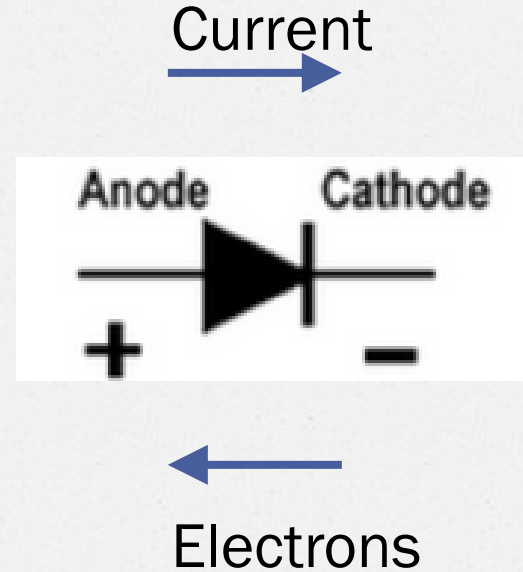

Light Emitting Diode

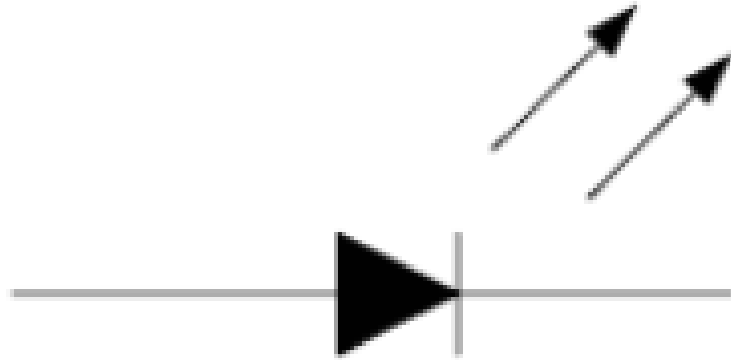
Same as diode but also releases energy (as light)



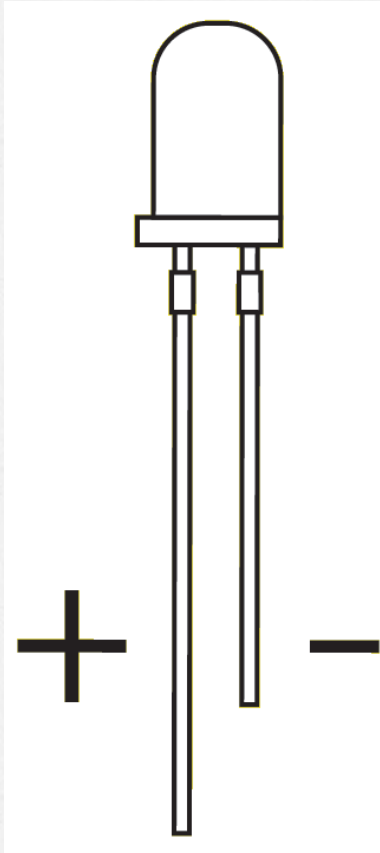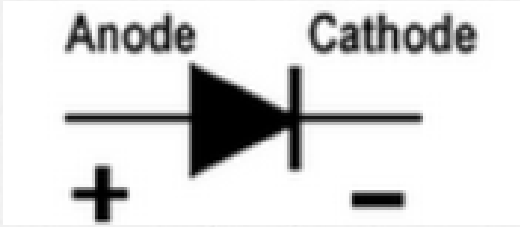


Just like battery,
the (+) side is
longer


Diode

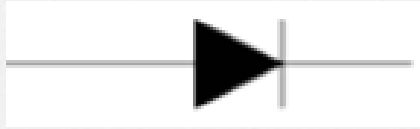

LED

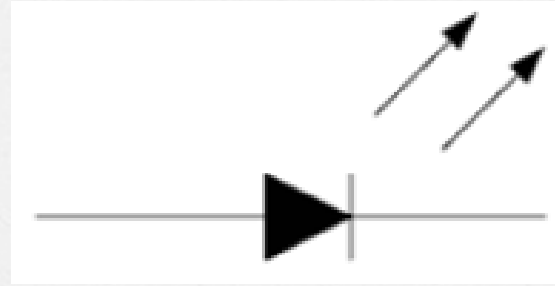



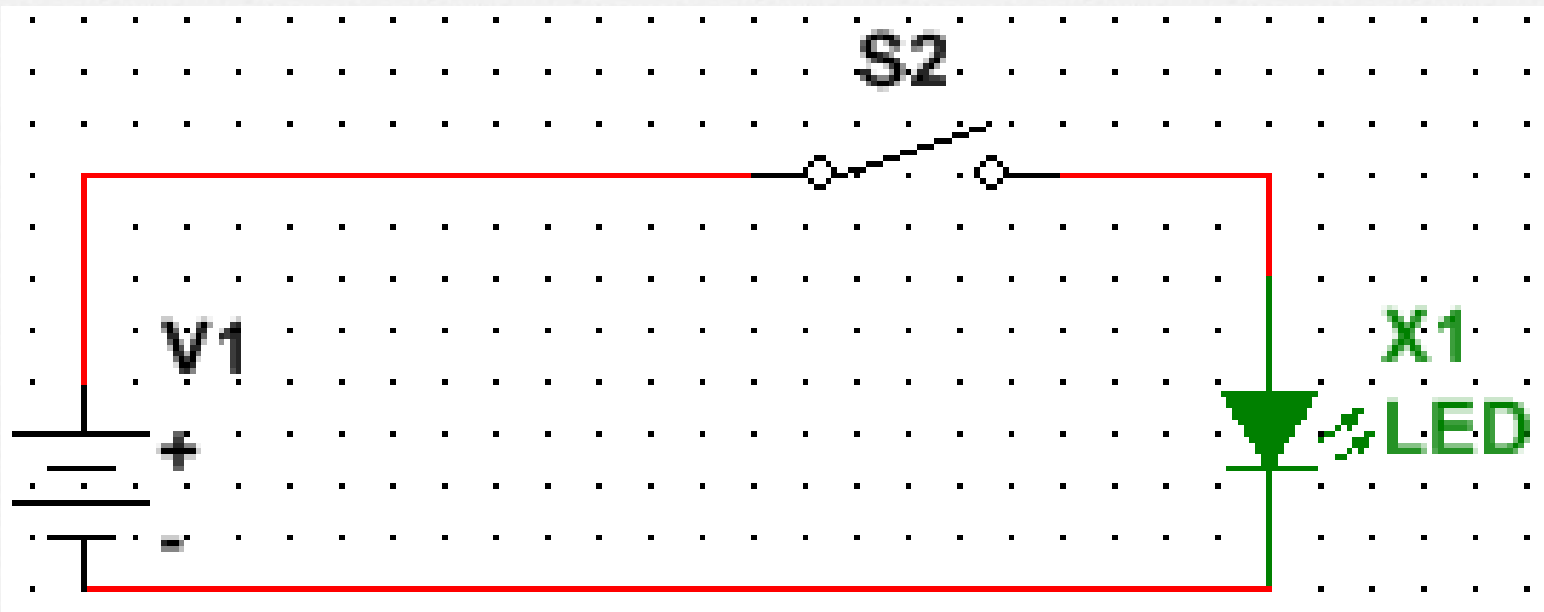



Review Switches

SPDT switch



OR



Single Pole Double Throw

One pole in the middle


It has two options for
where to connect
(double throw)

DPST switch

Double Pole Single Throw

TWO poles!

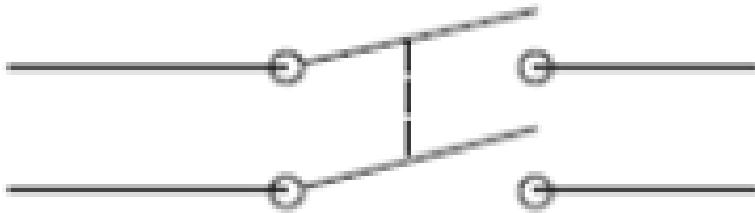But each pole only has
place to go (single
throw)




Looks like two SPST
switches glued together

DPDT switch

Double Pole Double Throw



OR


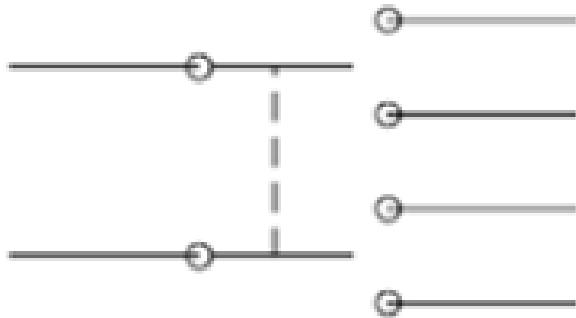


Two poles again

Each pole has TWO options for where to connect (double throw)


Looks like two SPDT switches glued together

DPDT switch

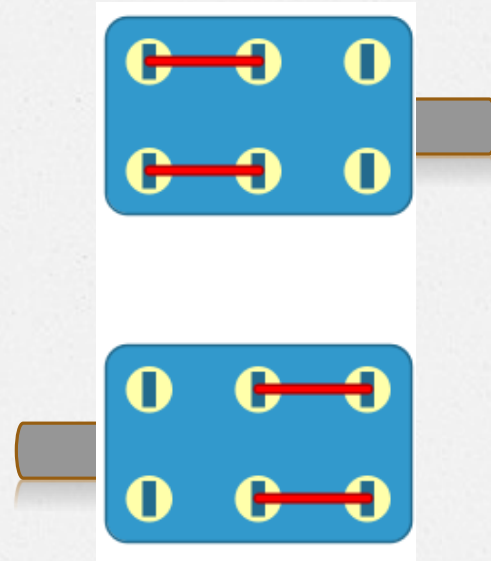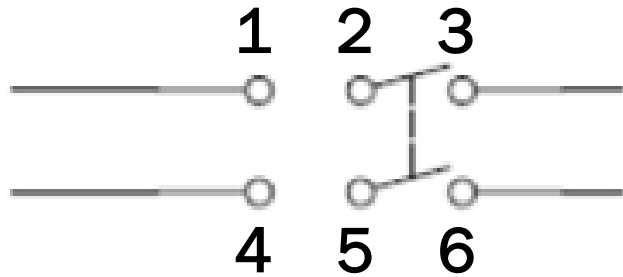



Practice Practice Practice...

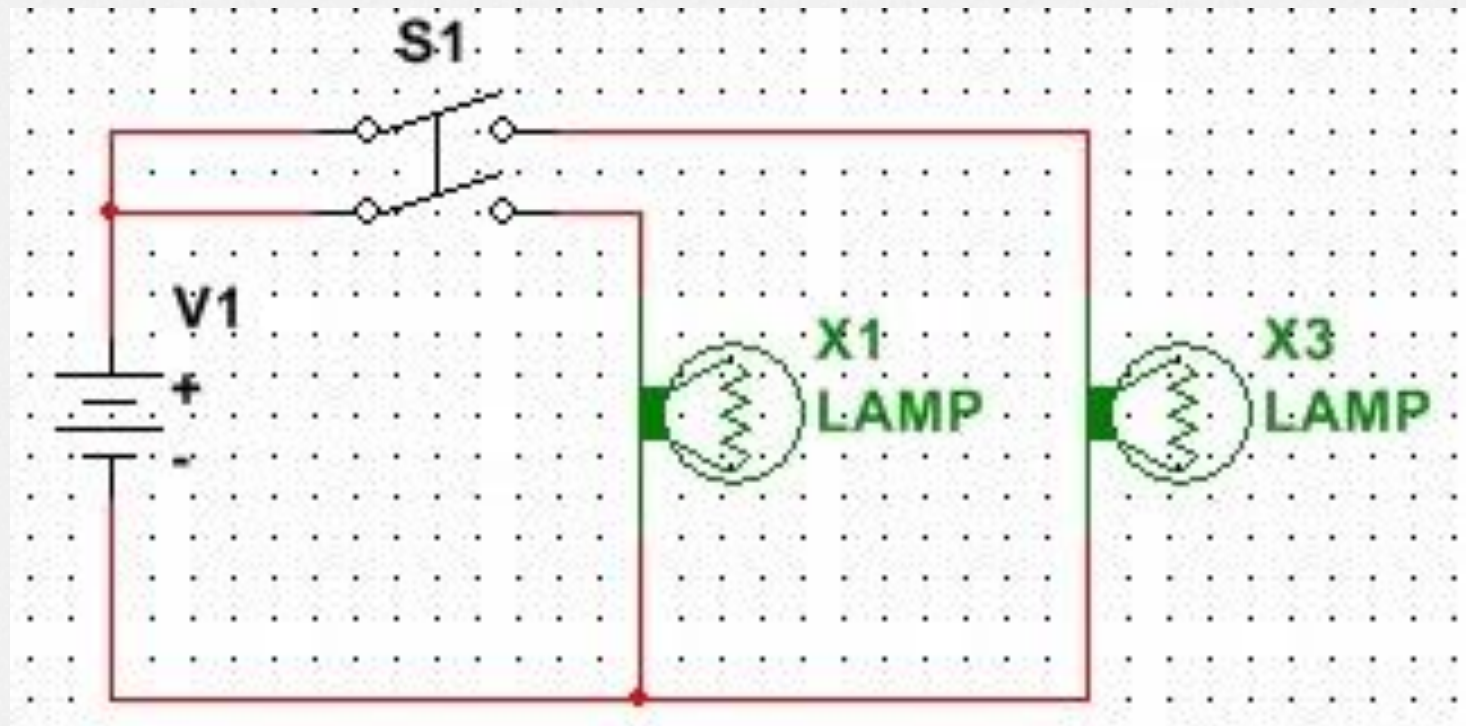


Variable Resistor

Normal resistor whose resistance can be changed.

Example use: “dimmer” switch




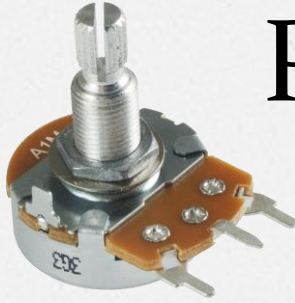


Potentiometer


A resistor with a movable “tap” in the middle.

Example use: “voltage divider”

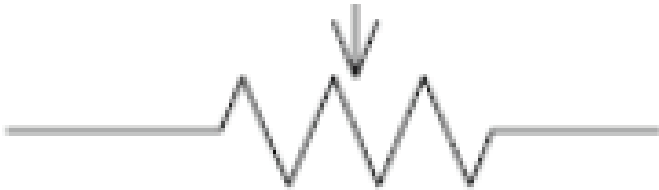

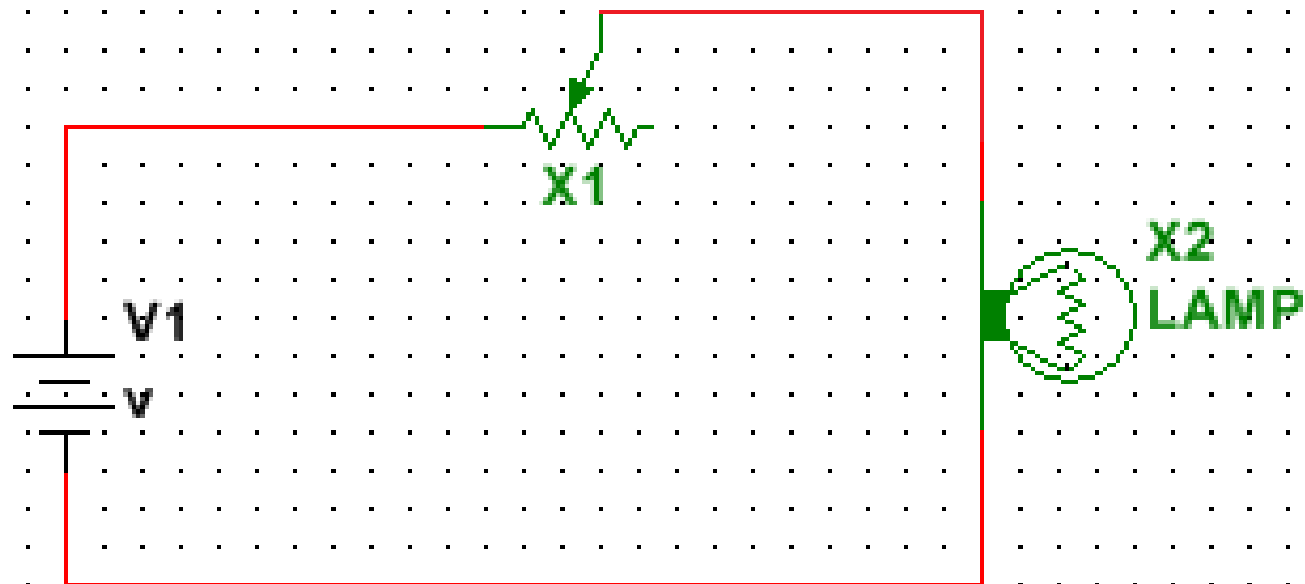Note: pots can be used as variable resistors (think how?)



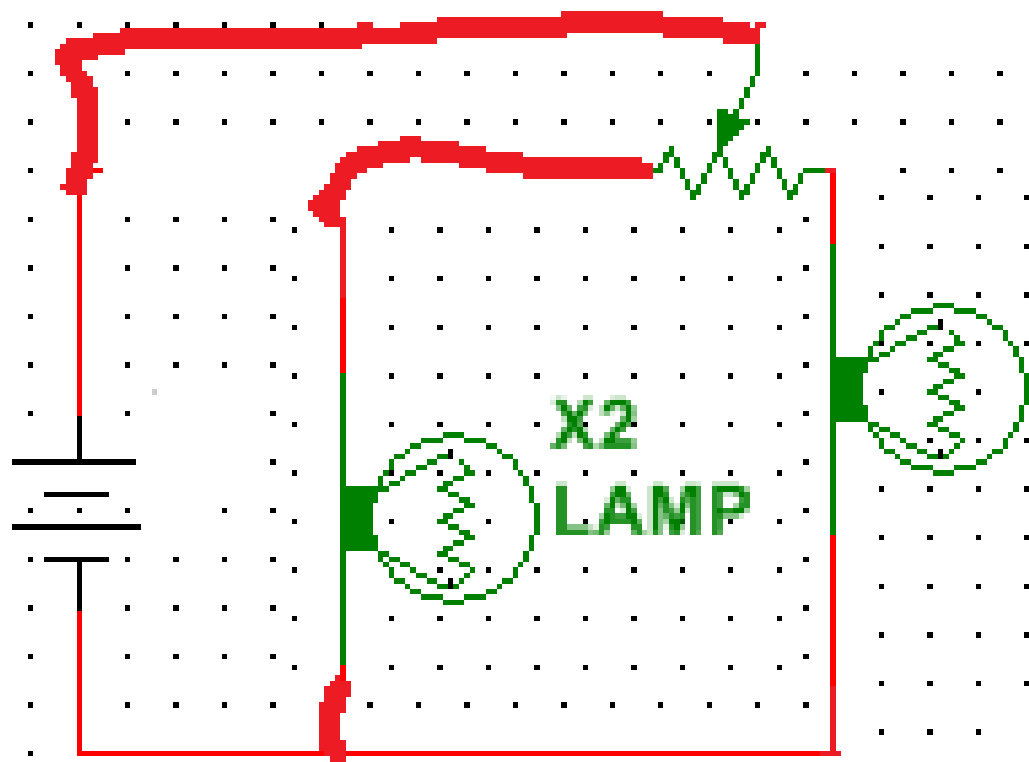



Measurment



DMM

Digital Multi Meter


Can measure voltage and current



DMM

Digital Multi Meter

Can measure voltage and current

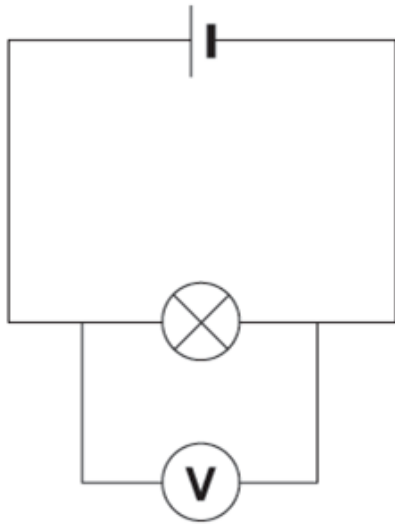

Voltage
measurements
must be done in
parallel




DMM


Digital Multi Meter

Can measure voltage and current

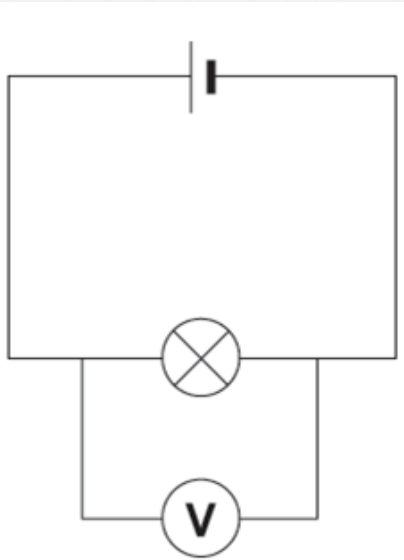Current measurements must be done in series



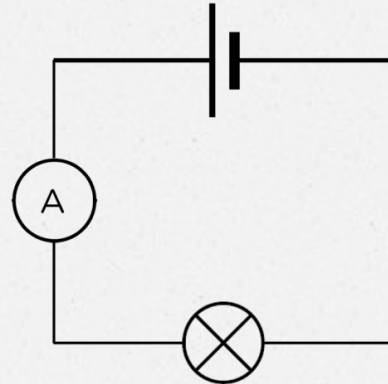Voltage
measurements
must be done in
parallel



DMM

Make sure to use the right setting

(A=amps, V=voltage, ...)

Don't use the "squiggly" line
settings (they are for AC circuits)

Also use to the right terminals


Always connect one lead to COM
(short for common)





CAPACITORS ARE NOT INCLUDED
IN CIRCUIT WIZARDRY 2025


Capacitor

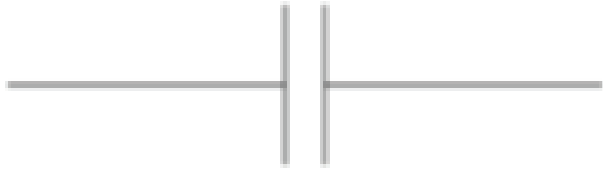


OR



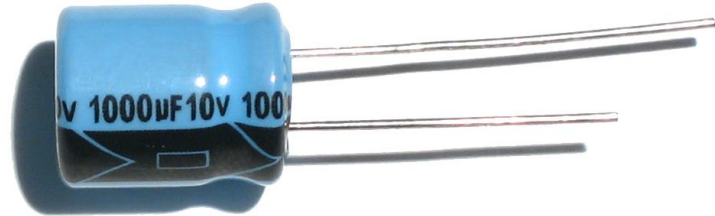Stores energy - it's like a temporary battery



POTENTIOMETER

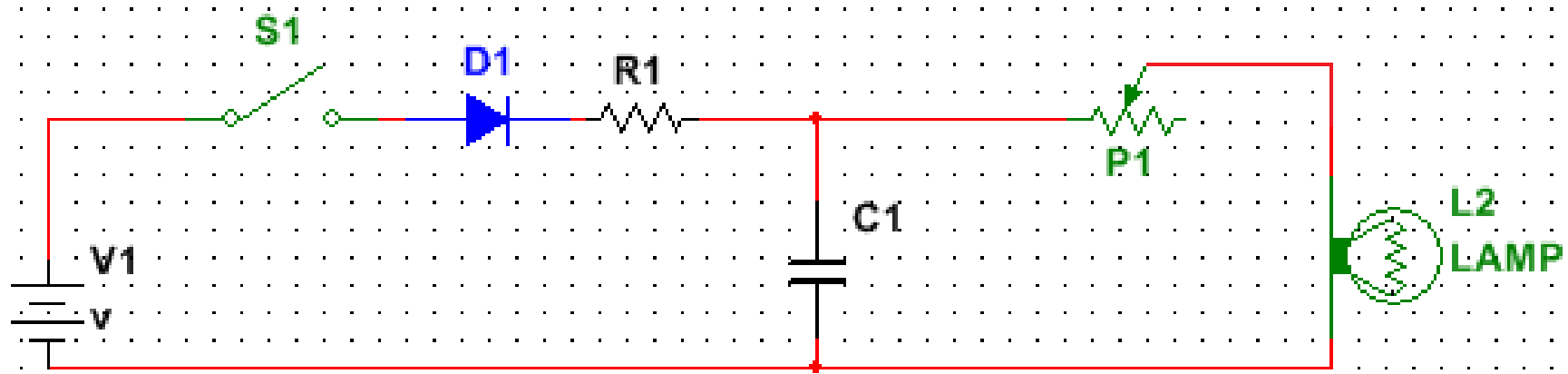



Flashcards




DMM


Digital Multi Meter

Can measure voltage and current

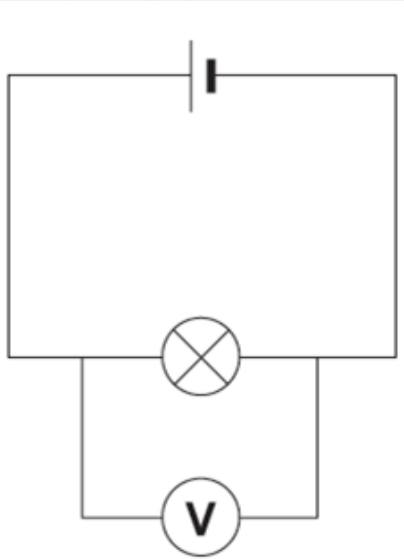Current measurements must be done in series



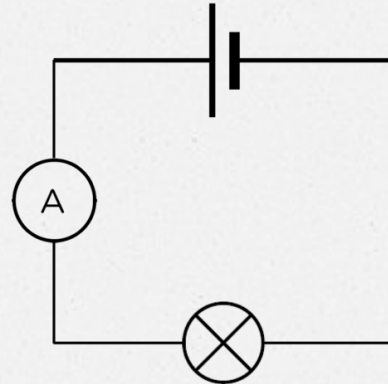Voltage
measurements
must be done in
parallel




Variable Resistor

Normal resistor whose resistance can be changed.

Example use: “dimmer” switch




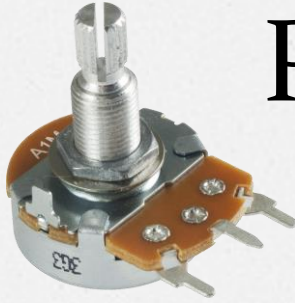

Potentiometer

A resistor with a movable “tap” in the middle.

Example use: “voltage divider”

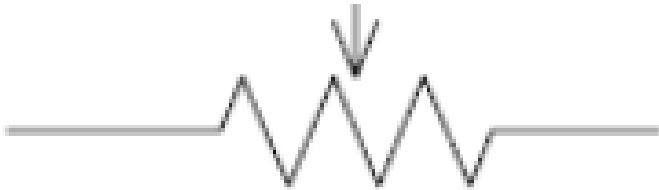

Note: pots can be used as variable resistors (think how?)


Capacitor



OR



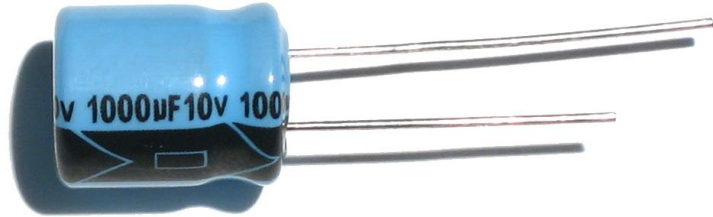Stores energy - it's like a temporary battery



To do at home :)

Make sure to:

Memorize flashcards

Build more circuits (start with the ones in this slideshow then be creative and build your own)

Check out these cool videos/apps:

[Link #1](#) – Another Circuit Builder (this one shows voltage and current)

[Link #2](#) – Falstad Circuit Builder (fairly advanced, it will make more sense after each workshop)

[Link #3](#) – C is for Capacitor